

16 Watt Bridge Amplifier

This circuit can amplify an audio signal by 16 watts.

16-W BRIDGE AMPLIFIER

