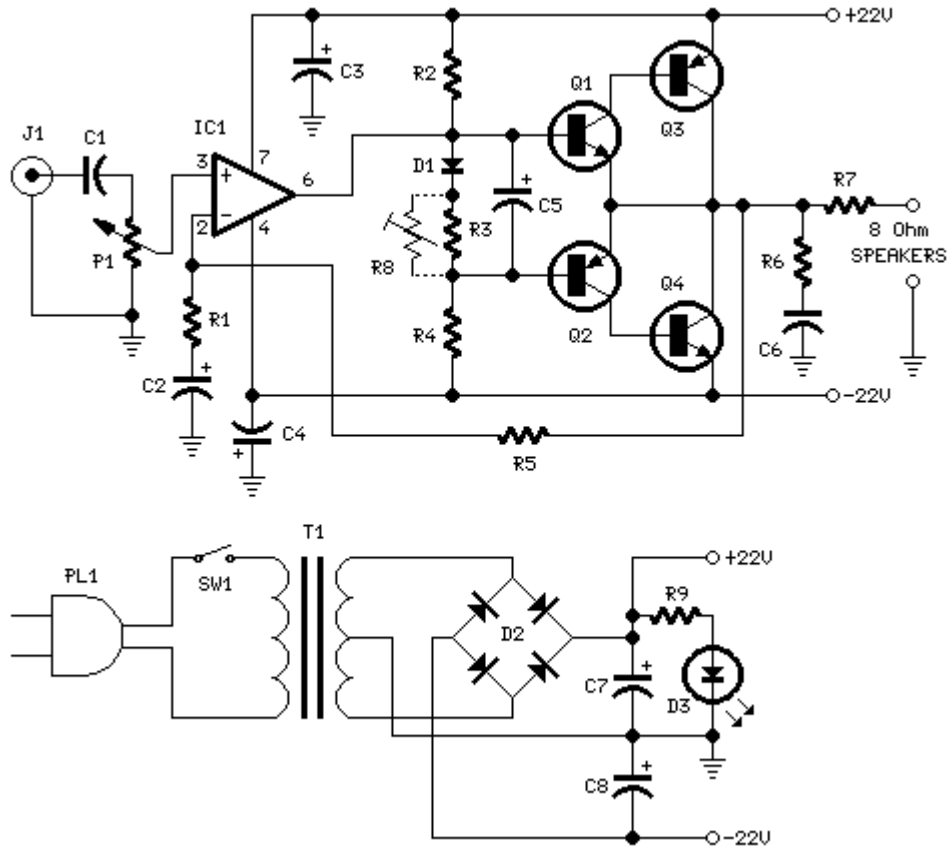


18W Audio Amplifier

High Quality very simple unit. No need for a preamplifier

Circuit diagram:



Amplifier parts:

P1 _____ 22K Log.Potentiometer (Dual-gang for stereo)

R1 _____ 1K 1/4W Resistor

R2 _____ 4K7 1/4W Resistor

R3 _____ 100R 1/4W Resistor

R4 _____ 4K7 1/4W Resistor

R5 _____ 82K 1/4W Resistor

R6 _____ 10R 1/2W Resistor

R7 _____ R22 4W Resistor (wirewound)

R8 _____ 1K 1/2W Trimmer Cermet (optional)

C1 _____ 470nF 63V Polyester Capacitor

C2, C5 _____ 100µF 3V Tantalum bead Capacitors

C3, C4 _____ 470µF 25V Electrolytic Capacitors

C6 _____ 100nF 63V Polyester Capacitor

D1 _____ 1N4148 75V 150mA Diode

IC1 _____ TLE2141C Low noise, high voltage, high slew-rate Op-amp

Q1 _____ BC182 50V 100mA NPN Transistor

Q2 _____ BC212 50V 100mA PNP Transistor

Q3 _____ TIP42A 60V 6A PNP Transistor

Q4 _____ TIP41A 60V 6A NPN Transistor

J1 _____ RCA audio input socket

Power supply parts:

R9 _____ 2K2 1/4W Resistor

C7, C8 _____ 4700 μ F 25V Electrolytic Capacitors

D2 _____ 100V 4A Diode bridge

D3 _____ 5mm. Red LED

T1 _____ 220V Primary, 15 + 15V Secondary 50VA Mains transformer

PL1 _____ Male Mains plug

SW1 _____ SPST Mains switch

Notes:

- Can be directly connected to CD players, tuners and tape recorders.
- Don't exceed 23 + 23V supply.
- Q3 and Q4 must be mounted on heatsink.
- D1 must be in thermal contact with Q1.
- Quiescent current (best measured with an Avo-meter in series with Q3 Emitter) is not critical.
- Adjust R3 to read a current between 20 to 30 mA with no input signal.
- To facilitate current setting add R8 (optional).
- A correct grounding is very important to eliminate hum and ground loops. Connect in the same point the ground sides of J1, P1, C2, C3 & C4. Connect C6 at the output ground.
- Then connect separately the input and output grounds at the power supply ground.

Technical data:

Output power: 18 Watt RMS @ 8 Ohm (1KHz sinewave)

Sensitivity: 150mV input for 18W output

Frequency response: 30Hz to 20KHz -1dB

Total harmonic distortion @ 1KHz: 0.1W 0.02% 1W 0.01% 5W
0.01% 10W 0.03%

Total harmonic distortion @10KHz: 0.1W 0.04% 1W 0.05% 5W
0.06% 10W 0.15%

Unconditionally stable on capacitive loads