

Intercom (Two-Way)

This circuit is for a full duplex intercom system. That is, signals can be sent either way. This makes it very useful for a security system in a house or even for different levels of the house. Since the operating voltage is 9VDC, it could easily be put in a vehicle, with a voltage regulator.

