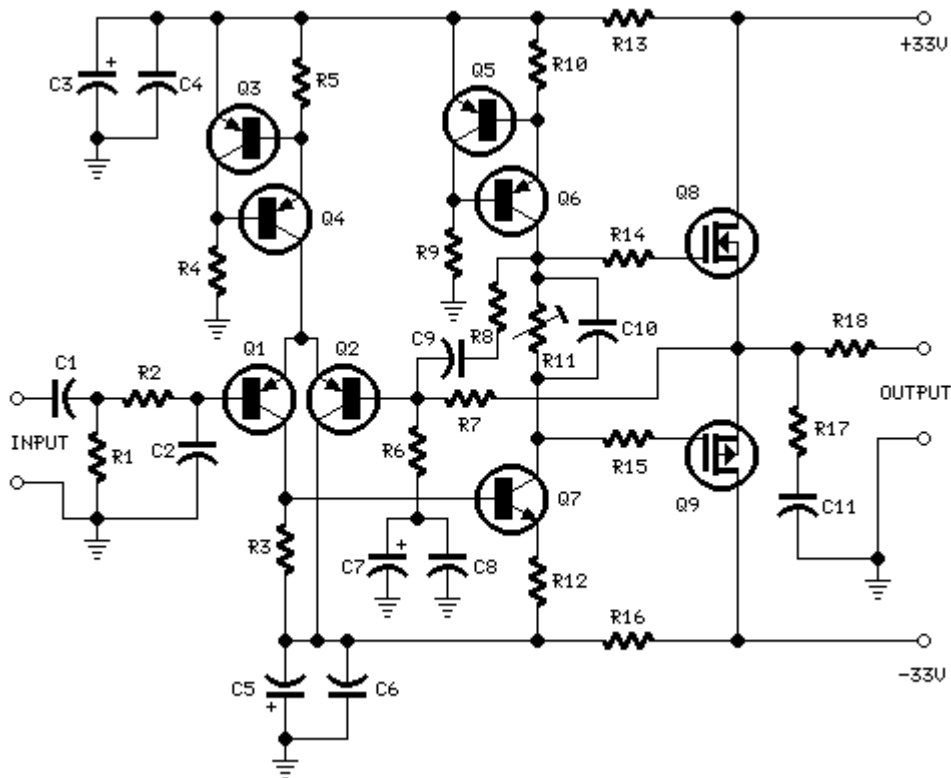


25 Watt MosFet Audio Amplifier

High Quality simple unit. No need for a preamplifier

Circuit diagram:




Parts:

R1,R4 _____ 47K 1/4W Resistors
 R2 _____ 4K7 1/4W Resistor
 R3 _____ 1K5 1/4W Resistor
 R5 _____ 390R 1/4W Resistor
 R6 _____ 470R 1/4W Resistor
 R7 _____ 33K 1/4W Resistor
 R8 _____ 150K 1/4W Resistor
 R9 _____ 15K 1/4W Resistor
 R10 _____ 27R 1/4W Resistor
 R11 _____ 500R 1/2W Trimmer Cermet
 R12,R13,R16 _____ 10R 1/4W Resistors
 R14,R15 _____ 220R 1/4W Resistors
 R17 _____ 8R2 2W Resistor
 R18 _____ R22 4W Resistor (wirewound)

C1 _____ 470nF 63V Polyester Capacitor
 C2 _____ 330pF 63V Polystyrene Capacitor
 C3,C5 _____ 470μF 63V Electrolytic Capacitors
 C4,C6,C8,C11 _____ 100nF 63V Polyester Capacitors
 C7 _____ 100μF 25V Electrolytic Capacitor
 C9 _____ 10pF 63V Polystyrene Capacitor
 C10 _____ 1μF 63V Polyester Capacitor

Q1-Q5 _____ BC560C 45V 100mA Low noise High gain PNP Transistors
 Q6 _____ BD140 80V 1.5A PNP Transistor
 Q7 _____ BD139 80V 1.5A NPN Transistor
 Q8 _____ IRF532 100V 12A N-Channel Hexfet Transistor
 Q9 _____ IRF9532 100V 10A P-Channel Hexfet Transistor

Power supply circuit diagram:

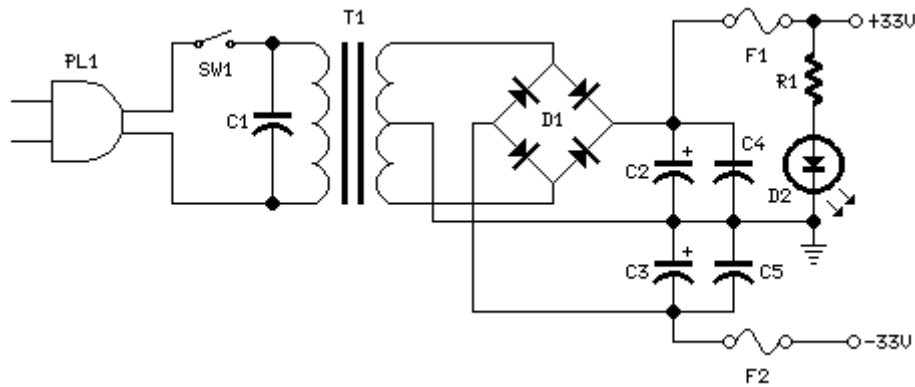

Parts:

R1 _____ 3K3 1/2W Resistor

C1 _____ 10nF 1000V Polyester Capacitor
C2,C3 _____ 4700 μ F 50V Electrolytic Capacitors
C4,C5 _____ 100nF 63V Polyester Capacitors

D1 _____ 200V 8A Diode bridge
D2 _____ 5mm. Red LED

F1,F2 _____ 3.15A Fuses with sockets

T1 _____ 220V Primary, 25 + 25V Secondary 120VA Mains transformer

PL1 _____ Male Mains plug

SW1 _____ SPST Mains switch

Notes:

- Can be directly connected to CD players, tuners and tape recorders. Simply add a 10K Log potentiometer (dual gang for stereo) and a switch to cope with the various sources you need.
- Q6 & Q7 must have a small U-shaped heatsink.
- Q8 & Q9 must be mounted on heatsink.
- Adjust R11 to set quiescent current at 100mA (best measured with an Avo-meter in series with Q8 Drain) with no input signal.
- A correct grounding is very important to eliminate hum and ground loops. Connect in the same point the ground sides of R1, R4, R9, C3 to C8. Connect C11 at output ground. Then connect separately the input and output grounds at power supply ground.

Technical data:

Output power: well in excess of 25Watt RMS @ 8 Ohm (1KHz sinewave)

Sensitivity: 200mV input for 25W output

Frequency response: 30Hz to 20KHz -1dB

Total harmonic distortion @ 1KHz: 0.1W 0.014% 1W
0.006% 10W 0.006% 20W 0.007% 25W 0.01%

Total harmonic distortion @10KHz: 0.1W
0.024% 1W 0.016% 10W 0.02% 20W 0.045% 25W 0.07%

Unconditionally stable on capacitive loads