

8 Watt Amplifier

This circuit can amplify an audio signal 8 watts.

