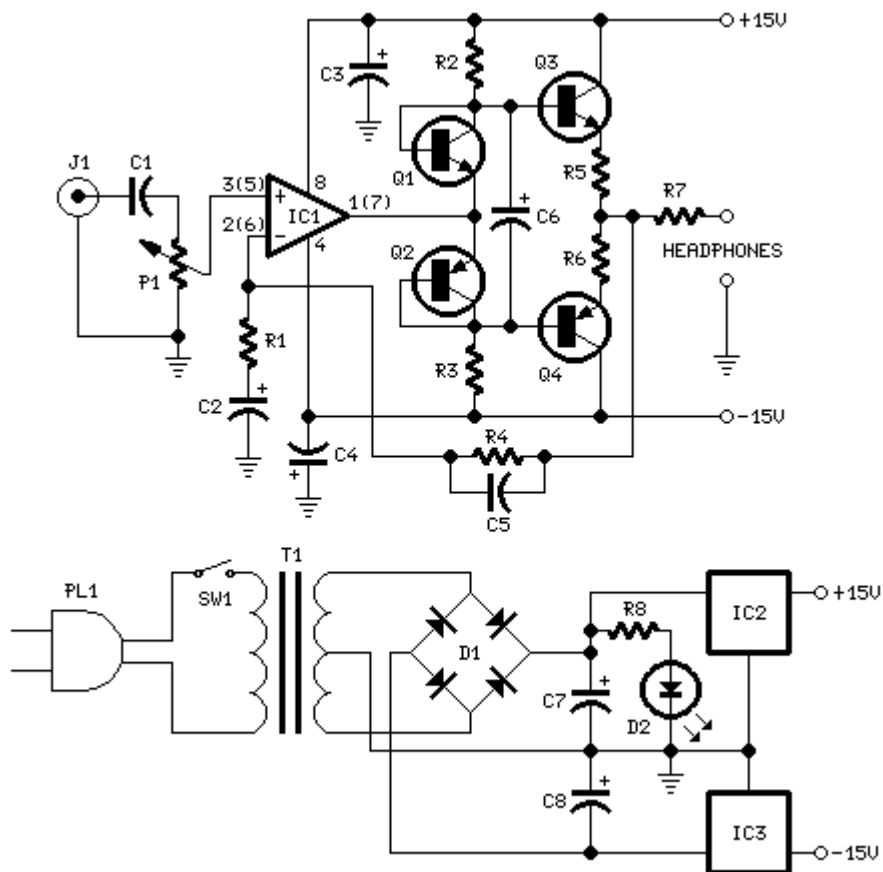


Headphone Amplifier

High Quality unit. No need for a preamplifier

Circuit diagram:



Amplifier parts:

P1 _____ 22K Log.Potentiometer (Dual-gang for stereo)

R1 _____ 560R 1/4W Resistor

R2,R3 _____ 10K 1/4W Resistors

R4 _____ 12K 1/4W Resistor

R5,R6 _____ 2R2 1/4W Resistor

R7 _____ 22R 1/2W Resistor

C1 _____ 1 μ F 63V Polyester Capacitor

C2,C3,C4 _____ 100 μ F 25V Electrolytic Capacitors

C5 _____ 22pF 63V Polystyrene or Ceramic Capacitor

C6 _____ 22 μ F 25V Electrolytic Capacitor

IC1 _____ LM833 or NE5532 Low noise Dual Op-amp

Q1,Q3 _____ BC337 45V 800mA NPN Transistors

Q2,Q4 _____ BC327 45V 800mA PNP Transistors

J1 _____ RCA audio input socket

Power supply parts:

R8 _____ 2K2 1/4W Resistor

C7,C8 _____ 2200 μ F 25V Electrolytic Capacitors

D1 _____ 100V 1A Diode bridge

D2 _____ 5mm. or 3mm. Red LED

IC2 _____ 7815 15V 1A Positive voltage regulator IC

IC3 _____ 7915 15V 1A Negative voltage regulator IC

T1 _____ 220V Primary, 15 + 15V Secondary 5VA Mains transformer

PL1 _____ Male Mains plug

SW1 _____ SPST Mains switch

Notes:

- Can be directly connected to CD players, tuners and tape recorders.
- Tested with several headphone models of different impedance: 32, 100, 245, 300, 600 & 2000 Ohms.
- Can drive old 8 Ohms impedance headphones, but these obsolete devices are not recommended.
- Schematic shows left channel and power supply.
- Numbers in parentheses show IC1 right channel pin connections.
- A correct grounding is very important to eliminate hum and ground loops. Connect in the same point the ground sides of J1, P1, C2, C3 & C4. Then connect separately the input and output grounds at the power supply ground.

Technical data:

Output voltage: Well above 5V RMS on all loads

Sensitivity: 250mV input for 5V RMS output

Frequency response: Flat from 30Hz to 20KHz

Total harmonic distortion @ 1KHz & 10KHz: Below 0.005% on 32 Ohms load and up to 4V RMS output (typical 0.003%)

Total harmonic distortion @ 1KHz & 10KHz: Below 0.005% on 100 to 2000 Ohms load and up to 5V RMS output (typical 0.003%)

Unconditionally stable on capacitive loads