
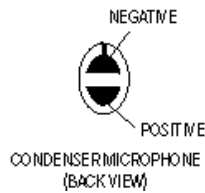
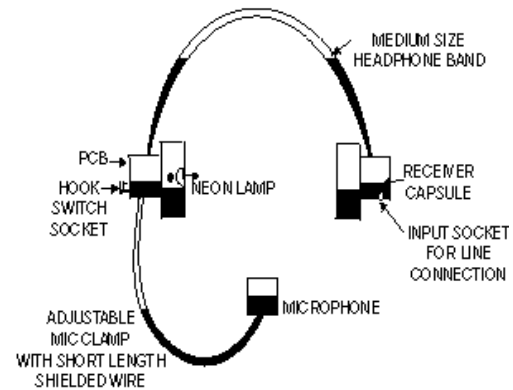


Telecom Headset

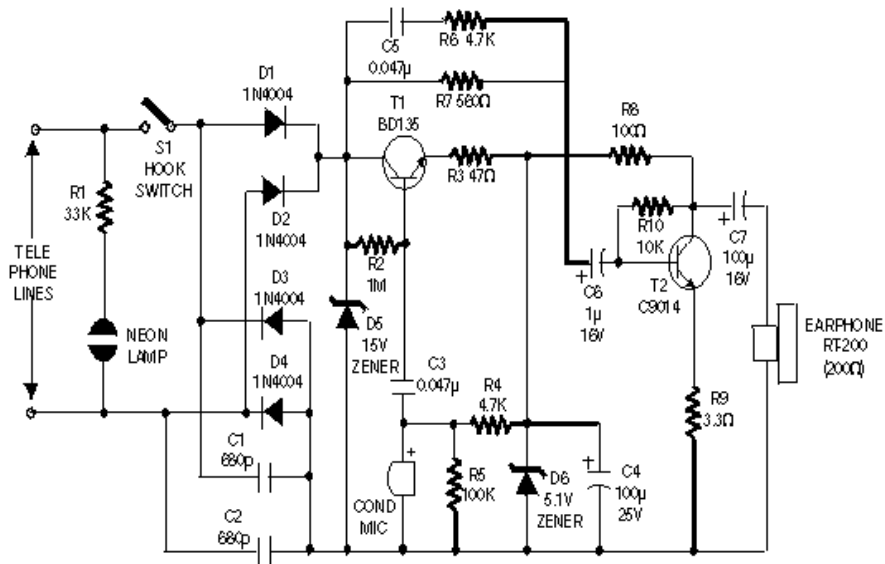This circuit is a cheap headset that can be used to hear telecom signals.



PROPOSED HEADSET