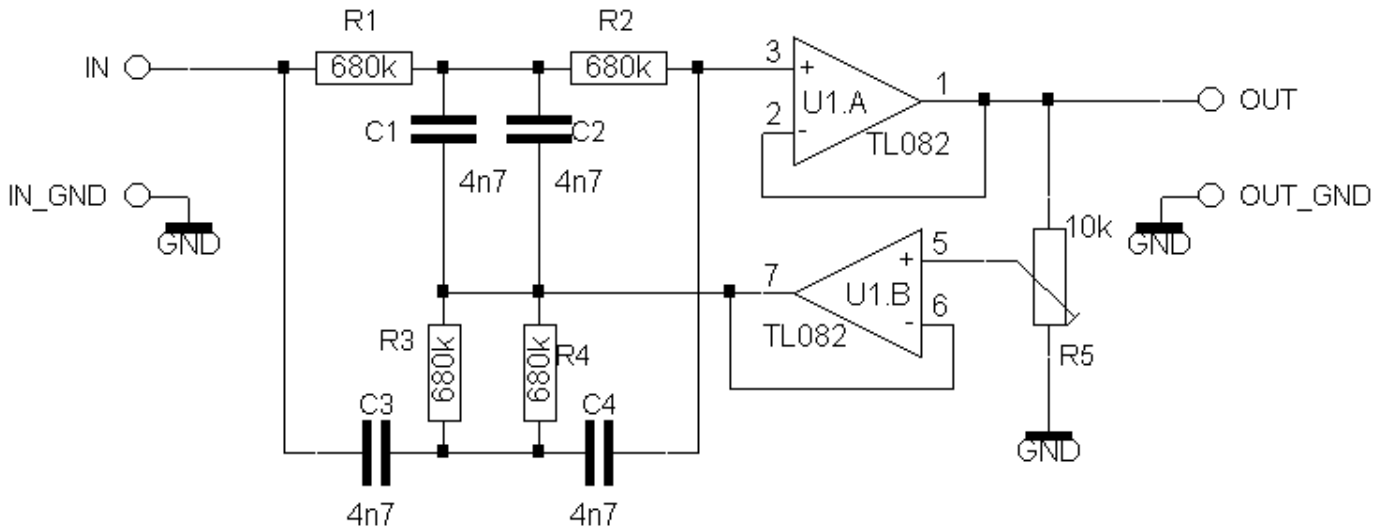


Twin T Notch Filter


Introduction

This filter allows you to remove frequency band from a signal. In the example below, we'll design a 50Hz notch filter. This allows us to remove the 50Hz hum picked up by, say, a microphone cord. Of course, it can be easily designed for 60Hz as well.

Schematic



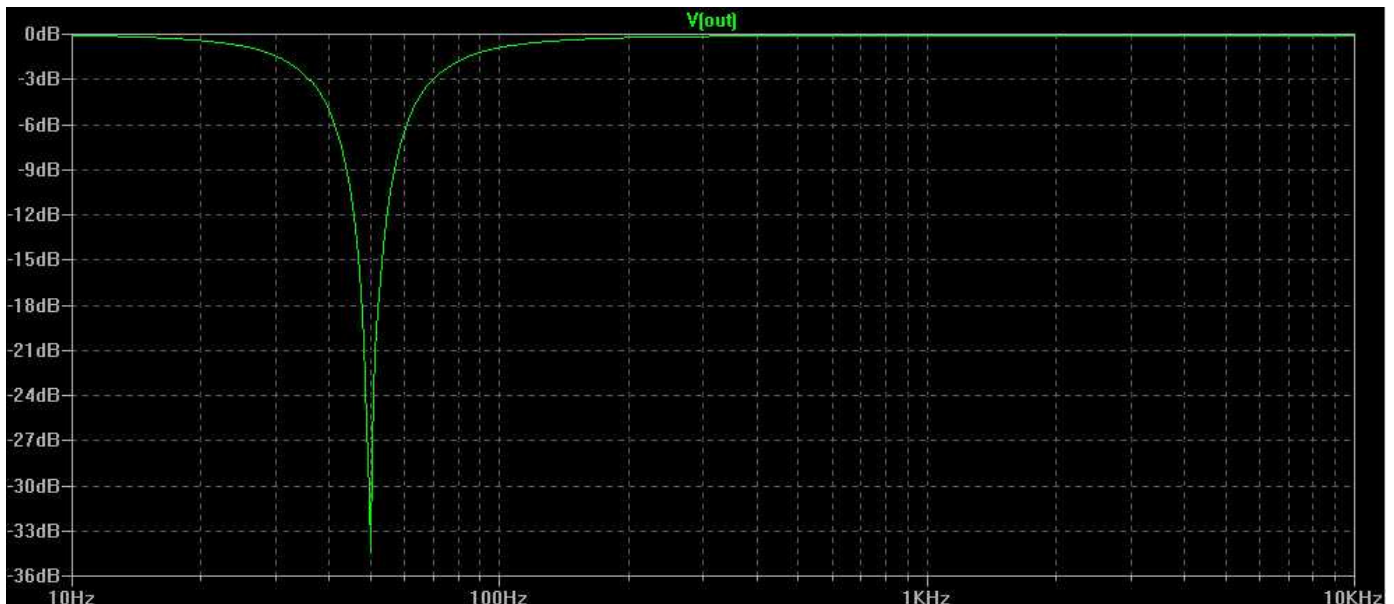The schematic clearly shows why this is called a "Twin T" filter. And a quick look at its frequency response explains why it's called a notch filter:



All resistors and capacitors must have the same value. Variable resistor R5 allows us to adjust the width of the notch.


The [notch frequency](#) is: $f=1/(4pRC)$, where $R=R3//R4$ (so $R1=R2=2R$) and $C=C1=C2=C3=C4$. In the schematic $R=340k$ and $C=4.7n$, so $f = 50Hz$.

Choosing components

The schematic above shows the component values for a 50Hz filter. If you want to build a 60Hz filter, all resistors must be 270k and all capacitors 10n.

Assembly

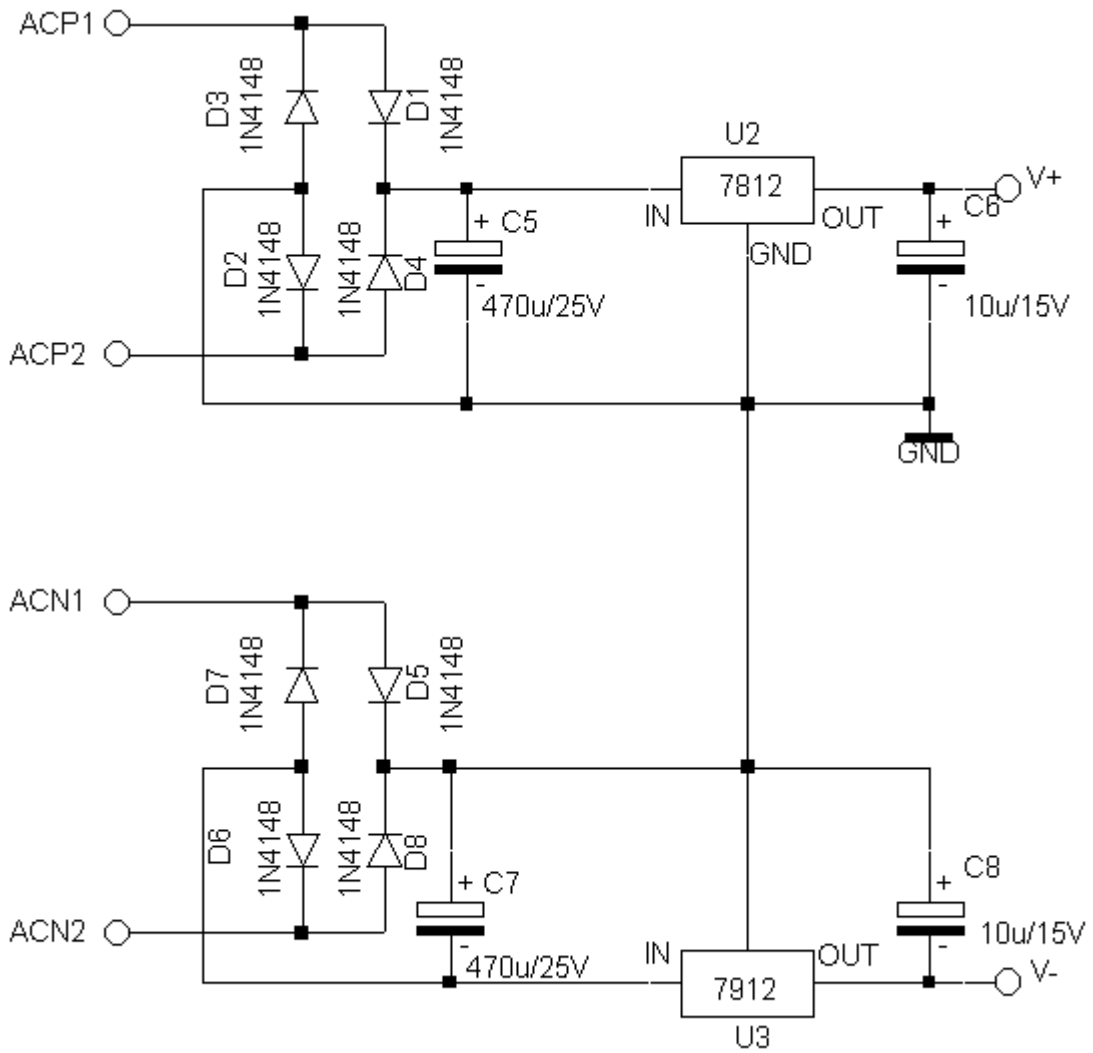The circuit is so small that the PCB has enough room for a simple power supply as well:



The component layout looks like this:

