

12V Light Dimmer

This circuit, powered by 12vdc, functions as a dimmer.

R1 = 100K C1,C3 = 10 μ F/16V

R2 = 100K C2 = 0.01 μ F, ceramic

R3 = 100K T1 = 2N4401

R4 = 100K T2 = TIP32

R5 = 3K9 U1 = LM358

R6 = 3K9 L1 = Lantern Bulb

R7 = 470 S1 = On-Off Switch

R8 = 100

R9 = 220, 1/2 watt

P1 = 5K

