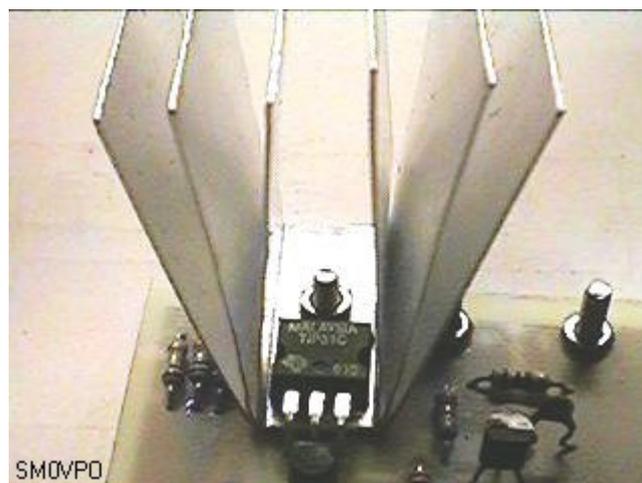
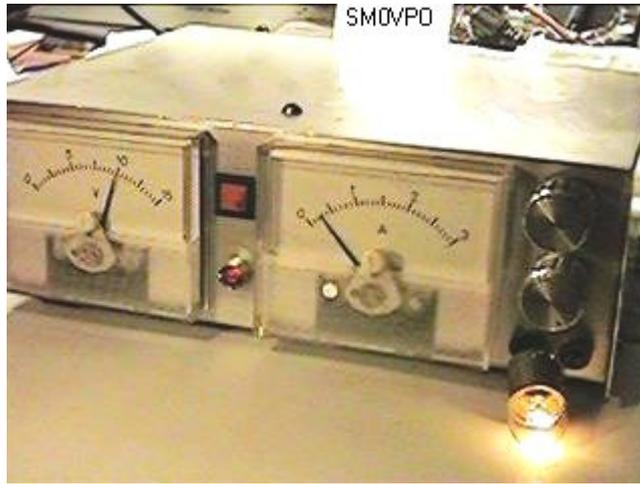




A full-wave rectifier provides the 18-volts input from a 15-0-15 volt mains input transformer. The diodes 1N5401 are rated at 3-amperes. At first sight, it would appear that 1-Ampere diodes, such as 1N4001, would suffice, but this is not the case. Although the average current through these diodes is a little over 500mA, the 2700uf input capacitor will be charged with short pulses, each considerably higher than 500mA. If the 2700uf capacitor were to be increased in value, then the rectifier diodes may need to be rated even higher. I used two parallel 47000uf in the prototype PSU, mainly because I wanted more output current so an additional regulator transistor is to be added. By the way, the supply smoothing capacitors are not mounted on the board. Note that the TIP31 output transistor MUST be fitted with a heatsink. With minimum output voltage (say, 0.1vDC) and an 18.1v pre-regulator voltage, the TR6 TIP31 output transistor will be dissipating $18v \times 1A = 18$ watts. If we allow the device temperature to rise TO 120°C then we can allow an increase of 90°C over the ambient room temperature. $90^{\circ}\text{C} / 18\text{watts} = 5^{\circ}\text{C per watt}$. A heatsink of 100 square cm is therefore required. If you wish to pull more current from this PSU then you will need a larger heatsink and change the value of Rx accordingly. Up to about 3-amperes is quite possible. TR6 may also be replaced with a darlington pair power transistor (such as TIP31 + 2N3055) if you want more than 3-Amperes, more attention will be required to other parts of the circuitry, such as the rectifier and reservoir capacitor.



The heatsink shown above is three pieces of thin aluminium sheet, 11cm x 3cm drilled with a 3mm hole dead centre. These are bolted between the PCB and the TIP31 transistor before any other components are mounted on the board. The fins can now be bent up to form six fins, each 5cm x 3cm or a total surface area of 180cm square. This is a little bigger than the calculation, but to over-engineer is not a fault (at least, not in my opinion). Here is the completed project.



The resistor R_x can also be used as a meter shunt for the output ammeter. I have used a 1mA meter with a series resistor selected to give a true current reading. Incidentally, take off the front scale of the meters, scan them and change the scale and lettering to suit your PSU. Then you can print the scale to paper and glue it over the existing meter scale. This gives a very professional finish. If you have an unsuitable scale ammeter, then open it up and cut the shunt wire between the two poles and then you have a small milli-ammeter or micro-ammeter that can be re-calibrated in this project.

I am presently updating the PCB foil pattern for this project, which I will include as soon as it is complete. I may perhaps offer this project in kit form, complete with heatsink, pots and all board-mounted components, but we will see what happens.

I hope that you have fun with this bench PSU, 73s from HARRY, Lunda, Sweden,