

This small FM transmitter gives up to 200-500m of range. Coil has 4 turns of 1mm Cu wire on a 10mm body (removed after winding). All caps below 1uF are ceramic.

Visit [Www.pcs-electronics.com](http://www.pcs-electronics.com) for more similar schematics...

