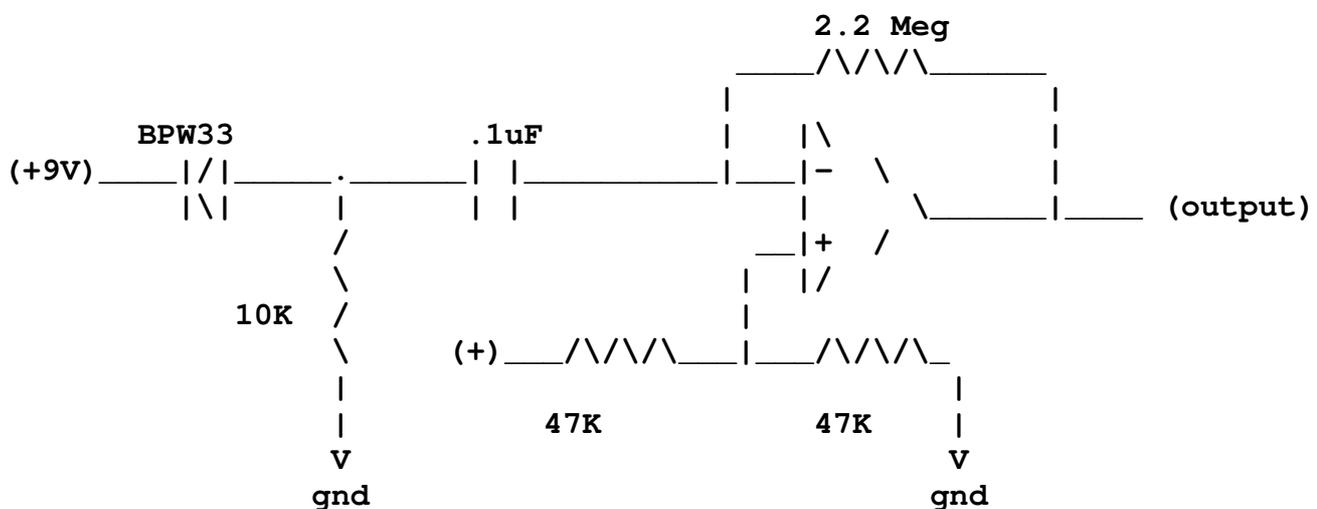


### "I to V" LO-NOISE PHOTOCCELL PREAMPLIFIER

The above schematic depicts a Current-to-Voltage converter circuit with a photodiode: if a 10 microamp signal comes from the photodiode, then a 2.2v signal will appear at the opamp output pin. The input is DC coupled for good lo-freq response. However, bright lights will overload the circuit. Here's an AC-coupled version:



I powered mine with a single 9V battery. Batt (-) goes to gnd and to pin-4, while batt (+) goes to pin-6 and to the (+) points on the schematic. The output signal will ride on 4.5VDC, so you might need to put a capacitor in series with the output to block the DC from your audio amplifier (my audio amp already had an internal capacitor in series with its input.) Either that, or use two 9V batteries wired as a standard Op-amp bipolar supply, and ground the (+) input pin of the op amp directly to the batteries' common connection.

If you build this "UFO Scope," definitely make a point to use it quite a bit before going hunting for "craft." You want to become familiar with the sounds of all conventional light sources, including lamps, headlights, aircraft, fires, and if you manage to crank the gain high enough, the twinkle patterns of various stars. That way you'll be able to point the device at the local version of "Marfa Lights" and either say "yeah, sure, it's just headlights," or possibly "holy \$#!%!, the

aliens modulate their ship-lights for voice communications!"

Spa fon! ;)

To greatly increase the sensitivity (by maybe 100x), replace the BPW34 with a phototransistor. I haven't tried this myself, so I can't recommend any particular phototransistor to try. Find one with a large active area if possible.

Another idea: build two sensors, install them in both eyepieces, and send the signals to stereo headphones. Then put an IR filter over one lens, and no filter (or an IR-cut filter) over the other (or perhaps magenta on one, and green on the other). With the view through both eyepieces totally blocked, this would be harder to aim, but it would let you HEAR THE COLORS of the lights as stereo audio information inside your head. Multiple colors should sound like various separate "instruments" located in the widely spread "orchestra." If the light source was changing colors, this might sound very interesting. At the very least, it would give you more clues for recognizing mundane light sources. Incandescent lights would be loud in the IR earpiece only, while merc vapor lights would not.

If one of these audio photosensor circuits was attached to the eyepiece of a large telescope, might any interesting sounds be received? For example, the flame of a candle \*sounds\* like the low rush of a burning candle. If the nucleus of a comet contains wailing gas jets, occasional explosions, vibrating plasma, etc., perhaps some of the comet's reflected light will become modulated, and the original sounds in the comet's atmosphere could be extracted by the telescope and photodetector. If the gain of my circuits could be raised by orders of magnitude, it might become possible to monitor the moon at new (dark) phase, and pick up tiny brief sounds of lunar meteor strikes. Their brief flashes would sound like clicks. Star-twinkle, if it contains moving interference fringes, might do more than make rumbles and thumps, it might "ping" or "squeak." Lunar occultation of stars also might create brief audio tones because of interference patterns. And if significant numbers of amateur astronomers start listening to the sky as well as watching it, perhaps unexplainable noises will lead to new discoveries for conventional (non-fringe!) science.

So far I've not encountered any mysterious lights. I have found that my single opamp stage doesn't give enough gain to "hear" the dimmest of the visible light sources without burying them in noise, so it's time to modify the thing. Add some extra gain stages, bigger initial gain resistor, a few tens of picofarads across the gain resistor to prevent oscillation, maybe a phototransistor replacing the photodiode to give higher front-end gain, and perhaps sacrifice low-freq response by making it AC coupled, so bright lights won't drive the opamp's output to the rails. Or give up and start over by building a photomultiplier version.

- [BPW33 sensor \\$0.25](#), also [S1223 PIN photodiode](#)
- [Photodiode front ends](#) (pdf)
- [Sci.Electronics FAQ: Infra-red detectors](#)
- [The Marfa Lights](#)
- [Diode Optical Receiver](#)
- [Bob Pease: What's all this transimpedance amp stuff anyhow?](#)
- [Photodiode op amps](#) (TI)