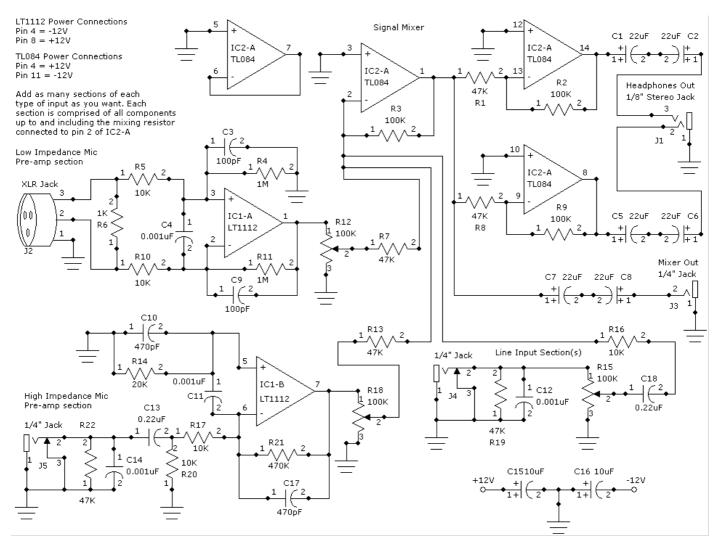
## **Another Mono Audio Mixer**

This mixer shows you how to make microphone pre-amps for low and hi impedance mics. Use the lowest noise opamp you can find that has similar characteristics to the LT1112 (although it is not too shabby itself). The board has extra line inputs and follows the schematic.



Another Mono Audio Mixer PC Board Component Side Shown

