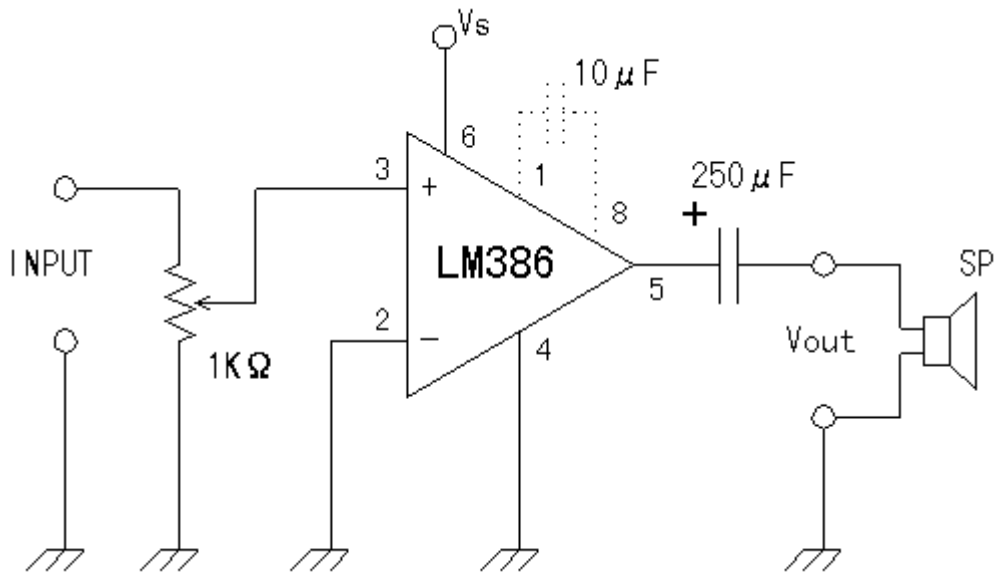


Simple amplifier



This is the low frequency power amplifier of which the penumbra article can be composed without using it hardly.
The about 660-mW output can be gotten with the 16-ohm speaker.

This circuit is used for the simple monitor and so on.
The impedance (4-ohm and 8-ohm, and so on), the output power of the speaker and so on are specified by the standard but are OK rather than strict. Because the sound cracks (warping) when presenting the output above the rating, it uses naturally within the standard.
When conscious of the timbre and the output power, it is better not to do the use of this circuit.

The use example : TV sound monitor circuit of [Frequency divider](#) and so on.

Data for LM386

Operating voltage range : 4 to 12V(LM386NN)
5 to 18V(LM386N-4)

Current in the standing still : 4mA(typ)

Package : 8 pins
Plastic DIL(code N)

The maximum rating (Ta=25°C)

V_S : 15V(LM386N) T_{stg} : -65 to +150°C
22V(LM386N-4) T_j : 150°C
P_D* : 660mW(LM386N) R_{th(j-a)} : 187°C/W(LM386N)
1.25W(LM386N-4) 100°C/W(LM386n-4)
V_{IN} : ±0.4V T_{pin} : 300°C.10sec
T_{opt} : 0 to +70°C * : Ta = 25°C

The electric characteristic (Ta=25°C)						
Symbol	Measurement condition		Min	Typ	Max	Unit
I _Q	V _S = 6V, V _{IN} = 0V			4	8	mA
I _{ib}	V _S = 6V, Term2,3 open			250		nA
G _V	V _S = 6V, f = 1kHz			26		dB
	It connects 10 μF with the interval of the term 1-8.			46		
P _{OUT}	V _S =6V, R _L =8ohm, THD=10%	LM386N-1	250	325		mW
	V _S =9V, R _L =16ohm, THD=10%	LM386N-3	500	700		
	V _S =16V, R _L =32ohm, THD=10%	LM386N-4	700	1000		
THD	V _S = 6V, R _L = 8ohm, P _{OUT} = 125mW f = 1kHz, Term1,8 open			0.2		%
R _{IN}				50		k-ohm
SVR	V _S = 6V, f = 1kHz, C _{BYPASS} = 10μF Term1,8 open			50		dB
BW	V _S = 6V, Term1,8 open			300		kHz