
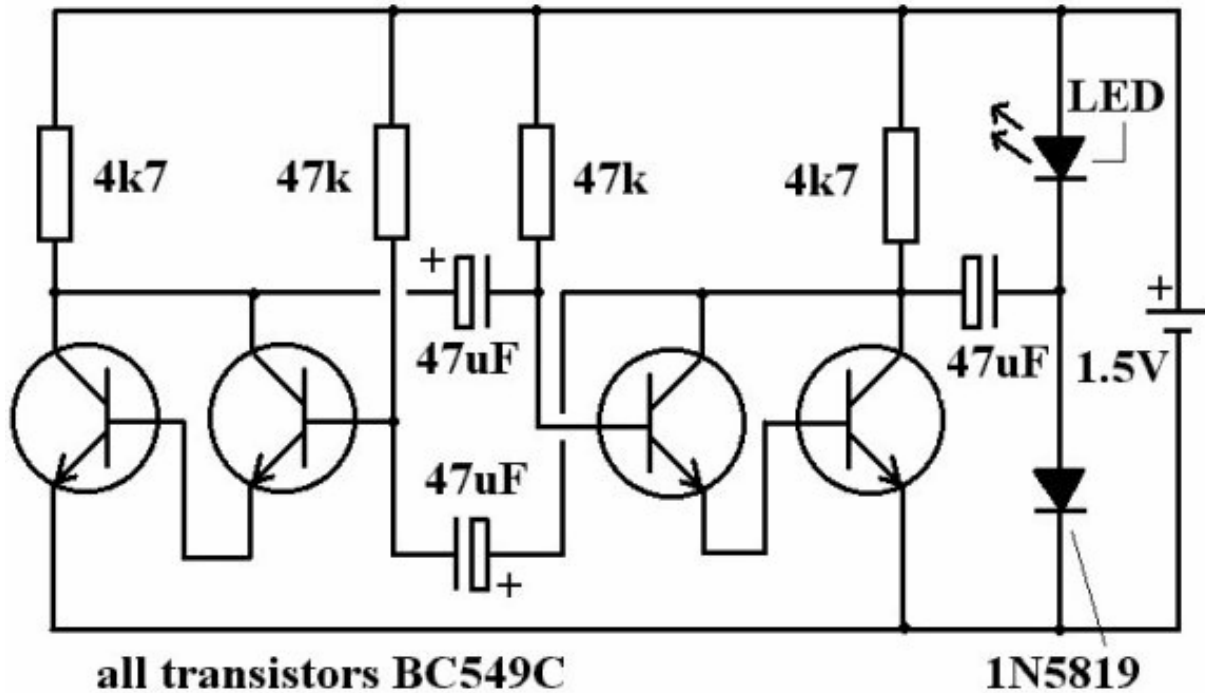

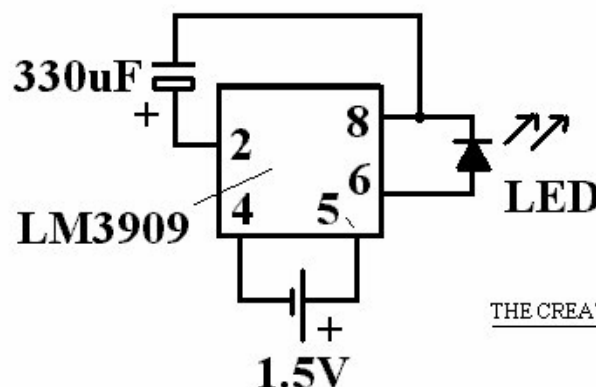
# Two Low Power LED Flashers


Both these circuits are remarkable in that they can flash an LED from a single 1.5V battery. A typical LED needs 2-3V to work properly and both these circuits include a voltage doubler to boost the voltage to drive the LED. Both circuits will operate continuously for several months on an alkaline AA battery and I have one circuit that has lasted for several years on an HP2 Duracell bat.


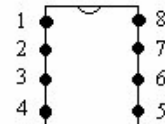
## LM3909 LED Flasher



numbering of LM3909 pins  
as viewed from above



THE CREATIVE SCIENCE CENTRE, 1997 JPH

The transistor circuit is included because of the recent difficulty in finding a supplier for the LM3909 flasher IC. The designer (Michael Kin, Electronics World, p.483, June 1998) claimed that the transistor circuit should operate for greater lengths of time than the IC circuit. See for yourself in the results below which show the battery voltage and flash rate comparisons for the two circuits left-on for a number of months.

Bat info: two AA 'Duracell Ultra' bats were used for the test taken from a two AA pack (bats. marked b.b.f MAR 2007).

### COMPARISON OF RESULTS FOR THE TWO FLASHER CIRCUITS

DATE	Transistor bat V	Trans. Flash/min	LM3909 bat V	LM3909 Flash/min	lab temp. (C)	comments
23/07/00	1.61	16	1.61	22	20	-
10/08/00	1.51	-	1.50	-	-	-
22/08/00	1.49	-	1.48	-	-	-
28/08/00	1.48	16	1.47	20	-	-
01/10/00	1.45	16	1.44	19	-	-
28/10/00	1.43	16	1.40	19	-	-
06/01/01	1.37	15	1.34	17	10	-
11/02/01	1.35	15	1.33	16	14	-
05/03/01	1.34	15	1.31	16	17	-
05/04/01	1.33	15	1.29	15	-	-
05/05/01	1.31	15	1.25	15	-	-
05/06/01	1.30	16	1.20	14	25	-
02/07/01	1.27	16	1.18	15	23	-
20/08/01	1.20	15	1.12	12	25	LM3909 brighter
16/09/01	1.20	14	1.07	10	20	LM3909 2 x bright
26/10/01	1.15	14	0.99	8	17	both dim
16/11/01	1.13	13	0.98	7	18	both dim LM3909 brighter
16/12/01	1.10	11	0.97	not flashing	10	transistor v dim LM3909 not flashing

(NOTE: ' - ' means data missing for this entry)

# LED'S

**SUMMARY** - There are so many different types of LED on the market (even of the same size and colour) , how do you tell the difference between them and which one you should use for your particular application? The simple tests described here compare the light output from 11 different types of 3mm red LED's.

## **INTRODUCTION**

Light Emitting Diodes (LED's) have replaced bulbs in many appliances (eg. Fridges, TV's, Radios, Videos, clocks, tapes players ... etc. etc.). They take very little electrical power, last for years without failing and are cheap. They are excellent little indicators for a whole host of experiments and gadgets. For examples see the experiments below:

[shake-a-gen  
rectifier and storage device  
sea water battery](#)

Although they are cheap and available there seem to be so many different types how do you know which one to use? The purpose of this little article is to compare a number of common LED's and see how they match up with each other. A question I wanted to ask was - are the LED's that are sold as very bright (eg. UltraBright) only useful in high power applications or are they just better all round ?

**The 11 LED's compared were:**

LED No.	Description	Code*	mcd (mA)	Series
(1)	standard red	55-0102	3 (10mA)	L-934
(2)	standard bright	55-0150	50 (10mA)	L-934
(3)	standard red	56-0740	3.2 (10mA)	L-34
(4)	superbright	56-0505	200 (20mA)	L-934SRD
(5)	superbright	72-8976	2500 (20mA)	L-934S
(6)	superbright	72-8978	400 (20mA)	L-934S
(7)	superbright	72-8980	1300 (20mA)	L-934S
(8)	ultrabright	56-0540	1000 (20mA)	L-934SRC
(9)	hyper red	72-8940	1300 (20mA)	L-934SURC
(10)	hyper red	72-8942	2000 (20mA)	L-934SURC
(11)	low I Super Red	56-0415	20 (2mA)	L-934L

NOTES: all LED's are 3mm red types, codes are the *RapidElectronics* order code, *mcd* = light o/p (in milli candela - is dependant on the current (mA in brackets)), all LED are made by *Kingbright* and the particular range (*series*) is shown for each LED in the last column.

## **TEST ONE - LOWEST OPERATING VOLTAGE**

In this test each LED was wired in series with a 390R resistor and the 11 circuits wired to a variable power supply. The voltage was set to about 3-4V and then slowly reduced till the first LED went out and the voltage measured. This was done till all the LED's went out. The results are of interest as a comparison only.

## RESULTS

LED 3 was the first to go out at 1.73V

LED 1 was next at 1.69V


LED 2 was out at 1.60V

The rest, LED 4 to 11 went out around 1.50V


## TEST TWO - LIGHT OUTPUT v VOLTAGE

With the same set up as in test one the voltage was set at 1.5, 2, 3, 4 and 5V (applied across each LED 390R resistor series circuit). The brightness for these 'constant' voltages were then compared.

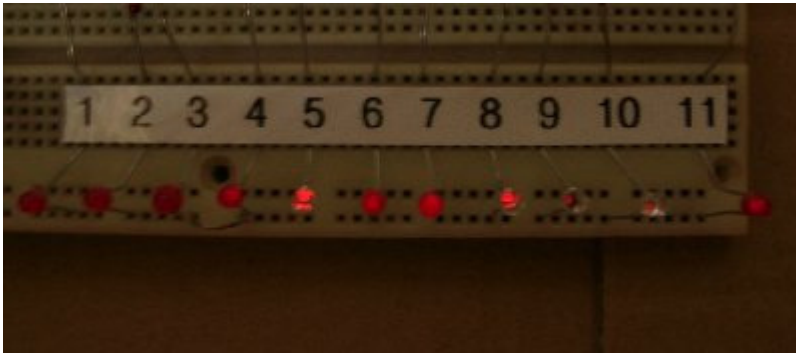
**In all the pictures shown below LED (1) is on the far left and they go through to LED (11) on the far right. Note: these pictures are only meant to give a rough indication of the relative brightness of the LED's.**



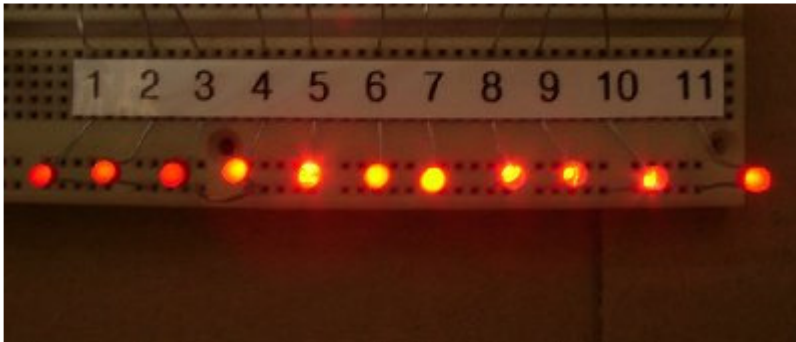
**Above:** Power supply = 1.5V. (390R series resistors). LED's (5) and (8) are brighter than (6), (7), (11) which are brighter than (4), (9), (10). Note: (1), (2) and (3) are off.



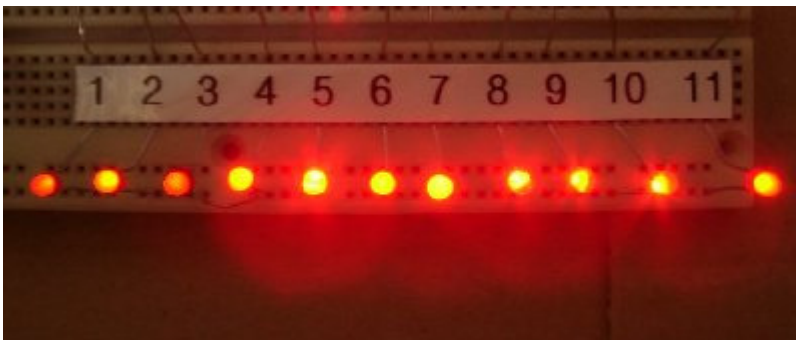
**Above:** Power supply = 2V. (390R series resistors). (5) to (9) are brighter than (4), (10), (11) which are brighter than (2), (3) which are brighter than (1).



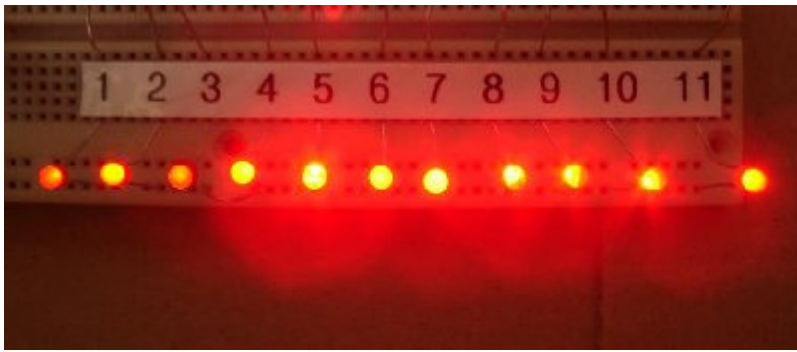**Above:** Power supply = 3V. (390R series resistors). (5) to (8) are about the same and brighter than (4), (9) to (11) which are brighter than (2), (3) which are brighter than (1).



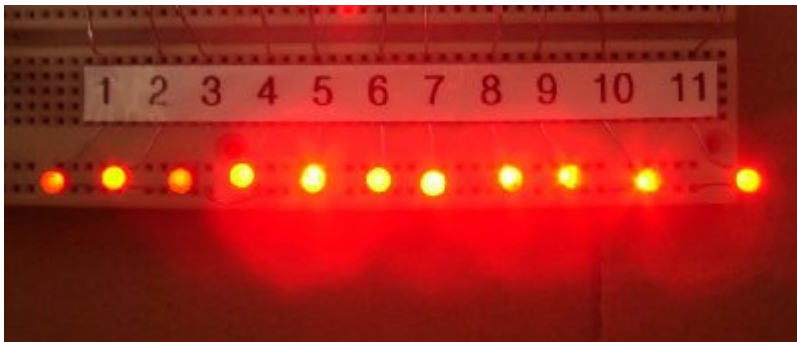**Above:** Power supply = 4V. (390R series resistors). (5) to (8) are brighter than (4) and (9) to (11) which are brighter than (1), (2) and (3).



**Above:** Power supply = 5V. (390R series resistors). (5) to (8) are brighter than (4), (9) to (11) which are brighter than (1), (2) and (3).

### **TEST THREE - LIGHT OUTPUT v CURRENT**

In these simple tests the series resistor limits, and roughly sets, the current flowing in each LED circuit (the current being dependent on the voltage). As all series resistors are the same value all the LEDs will have very nearly the same current flowing. As a last test I checked to see the effect of making sure each LED was being supplied with exactly the same current. This was done by wiring each LED with a fixed and preset resistor in series (390R + 1k variable) and the preset was adjusted so that each LED had the same current flowing in its own circuit (for the particular voltage applied to the system). This way each LED was adjusted independently to have the same current flowing. The procedure was repeated for 1, 2.5 and 5mA and the light output compared for the LEDs.

### **RESULTS**

There was no major difference from the results in test 2 above.

### **SUMMARY**

Although all LEDs No. (5) to (8) are very much in the lead as far as light output is concerned the all round best is probably the *superbright LED No. 5*. These high output LEDs are far better than the standard red LED (1) and seem to give out more light on lower voltage and less current (less power overall) than the standard. These LEDs will work very well in the Sea water battery and the shake-a-gen (and especially good in the shake-a-gen 'storage device') experiments.

## **ABOUT LED's**

A diode is a two wire component that only passes current when the voltage is applied correctly across it. Reverse wiring passes no current and for small voltages the device will act as a standard diode but it will brake down when higher voltages are applied. The LED, or Light Emitting Diode produces light when a current (usually 1-20mA) is passed through the device in the forward direction.

Unlike a resistor, the current flowing through a diode is not linearly dependant on voltage. In fact the current will go up exponentialy with the applied voltage. This means that at the 'light turn on' voltage (say 1.8V) a small current might flow (~10mA) but the applied voltage has only to increase by a few 0.1V's and the current can rise considerably (~100mA's). The current therefore needs to be limited to stop the LED burning out. This is simply done using a series 'dropping' resistor. The value of the resistor is given by the supply voltage minus the LED voltage (ca. 2V) divided by the LED current (~10mA), or roughly 100R for every volt, (ie. roughly 600R for 6V and 1k for a 9V battery). You can play around with the value by a factor of 2 or so to get more light o/p, its not too critical for most LED's (apart from the very high power ones).

---

## **THE CREATIVE SCIENCE CENTRE**

Dr Jonathan Hare, Room 3R253, Chichester Bldg. CPES, The University of Sussex  
Brighton, East Sussex. BN1 9QJ. 01273 606755 x3171

[home](#) | [diary](#) | [whats on](#) | [CSC summary](#) | [latest news](#)