

Super-Ear Audio Telescope

Tom Merryfield



Listen more clearly to those distant sounds

SUPER-EAR has been designed to incorporate a home-constructed parabolic element which boosts the sensitivity of an electret microphone for picking up sound at a distance. For example, as utilised in wildlife studies and, dare it be said, for eavesdropping on conversations from afar!

Because the microphone is securely held in copper tubing, impact and vibrational sounds through a barrier can also be detected to a certain extent. It was found with the prototype, that so long as a few precautions are followed, the results are comparable to those from a commercially produced device.

Parabolic Theory

Most readers will be familiar with satellite dish antennas in the shape of a parabola. Whereas a true parabola has a precise mathematical definition, most items approximating to this shape and with a reflective surface can be used to “catch” sound.

As shown in Fig.1, sound waves travelling more or less parallel from a distant source strike or “illuminate” the parabolic element. These in turn are re-directed to a focal point, X, at which the microphone is placed. In effect, this captures the targeted audio.

Although the focal point varies with different parabolas, the pick-up power of the microphone is considerably boosted since more sound waves are available from a particular source. The received input signal is then amplified as smoothly as possible by a sensitive circuit.

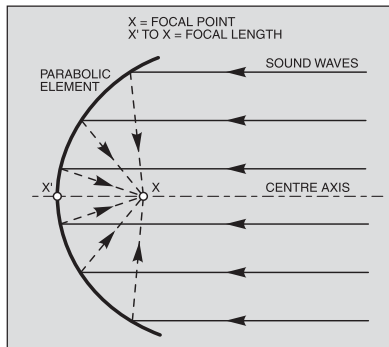


Fig.1. Properties of a true parabola

Circuit Description

In order to adequately amplify the input signal, the circuit consists of both pre-amplifier and audio amplifier stages. Referring to the full circuit diagram for the Super-Ear Audio Telescope in Fig.2, the electret microphone, MIC1, is powered

via resistor R1, which behaves as its load. The signal produced by MIC1 is a.c. coupled via capacitor C1 to the base of *npn* transistor TR1.

The network around TR1 forms the pre-amplifier stage. Resistors R2 to R5 bias it for linear amplification. The BC109C chosen is ideal for low noise audio applications such as this, offering more than adequate gain, although other general purpose high gain *npn* transistors will work in this design.

Any instability at this stage could distort signal processing throughout, hence the inclusion of capacitors C2 and C4. Capacitor C6 provides thermal compensation in the emitter circuit. Capacitor C3 and resistor R6 decouple the stage from disruptive power supply variations.

Audio Amplifier

Capacitor C5 couples the preamplified signal to level (Volume) control VR1, from where it is fed via C7 to IC1 input pin 3. The circuit around IC1 forms the audio amplifier stage. Capacitor C8 acts as an audio filter and the value quoted can be varied up to several nanofarads.

The LM386N audio amplifier i.c. has been chosen for IC1 because it is relatively easy to use and provides a smooth gain of over 200 (set by capacitor C9).

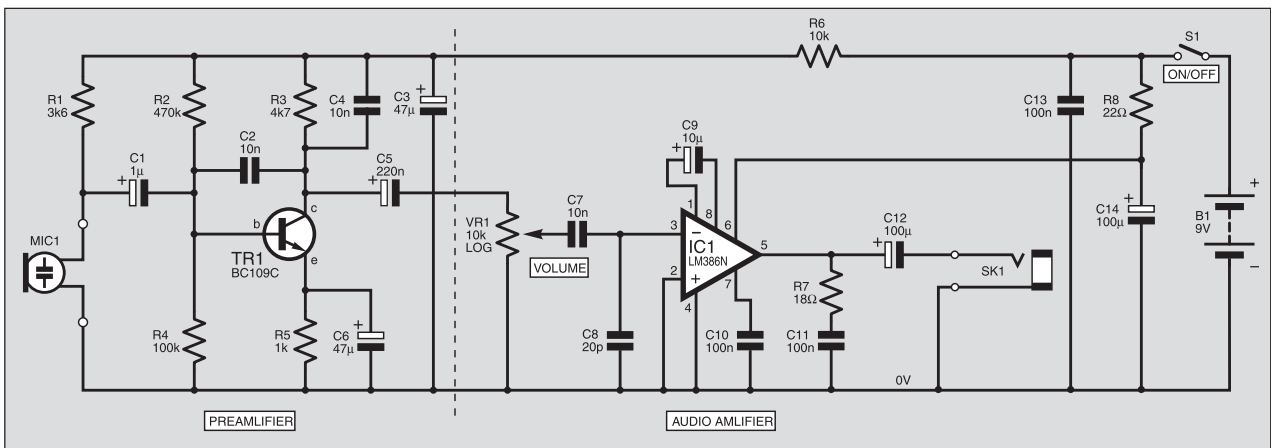




Fig.2. Complete circuit diagram for the Super-Ear Audio Telescope. This circuit is built on two circuit boards; preamplifier and audio amplifier

Table 1: Perception of Sound Intensity

| Source | Decibels* | Perception |
|--------------------|-----------|----------------|
| – | 0 | Silence |
| Rustling Leaves | 10 | Barely Audible |
| Soft Whisper | 20 | Quiet |
| Conversation | 60 | Audible |
| Factory | 80 | Fairly Loud |
| Construction Noise | 110 | Very Loud |
| Rock Concert | 120 | Pain Threshold |

* Decibels, perceived level varies with frequency

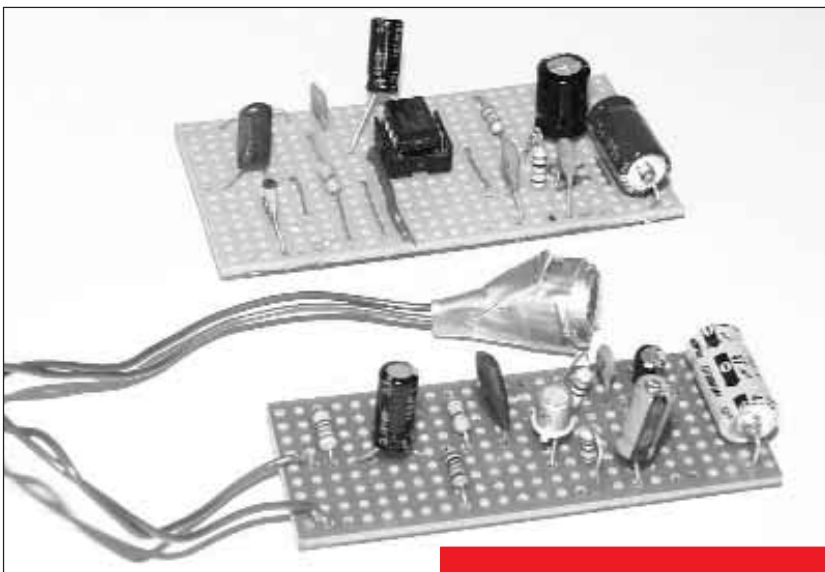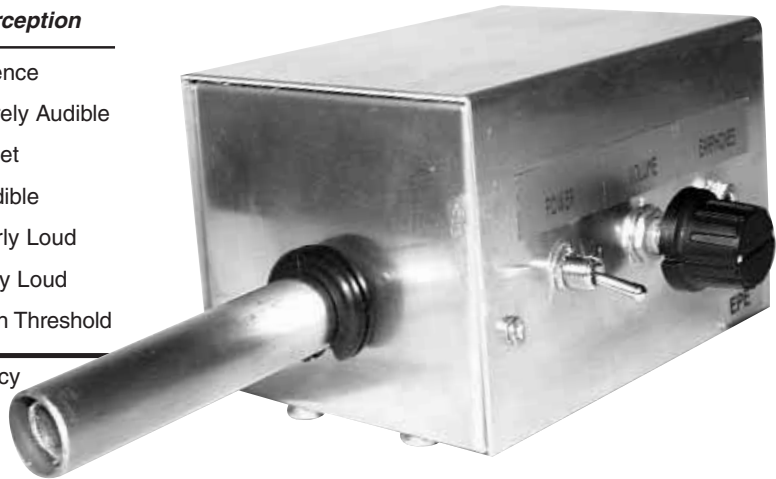Note that the human ear tends to perceive higher frequencies more easily



The two prototype circuit boards, with the tape-insulated Mic. between them. Differs slightly from the final unit

Most of the external components for IC1 are needed for stability. Capacitor C13 caters for variations in the supply voltage and is used on the main amplifier board, as opposed to the preamplifier board.

With IC1's output impedance being 64 ohms, Walkman-type headphones are preferable to speakers. This also avoids the problem of "telephony" which can hamper performance.

Construction

The prototype was built on two separate stripboards for several reasons. Firstly, both stages are isolated, which helps minimise problems with spurious feedback, whilst making fault-finding easier. Secondly, because the project is handheld, compactness is an issue. Two smaller circuit boards can be used to make the most of the available space.

The component layouts and track cutting details for the two stripboard assemblies are shown in Fig.3. Assemble the boards in the usual order of ascending component size, having first correctly cut the tracks where required.

Ensure that the electrolytic capacitors and the semiconductors are inserted the correct way round as shown. Use a socket for IC1, but do not insert the i.c. until the assembly has been completed and checked for accuracy.

Note that the electret microphone insert is also a polarised device. Its case is internally connected to one of its pins, to which the 0V connection should be made. The wiring to the microphone should not exceed about 140mm in length.

Testing

The circuit should be fully tested before housing it in a metal case. It is suggested that the main amplifier is tested first, without it being connected to the preamplifier.

When the amplifier is powered, touching the middle lug (wiper) of VR1 (or pin 3 of IC1) should produce a coarse buzz at

COMPONENTS

Resistors

| | |
|----|------|
| R1 | 3k6 |
| R2 | 470k |
| R3 | 4k7 |
| R4 | 100k |
| R5 | 1k |
| R6 | 10k |
| R7 | 18Ω |
| R8 | 22Ω |

All 0.25W 5% carbon film or better.

Potentiometer

| | |
|-----|------------------------|
| VR1 | 10k rotary carbon, log |
|-----|------------------------|

Capacitors

| | |
|---------------|---------------------------|
| C1 | 1μ radial elect. 25V |
| C2, C7 | 10n polyester (2 off) |
| C3 | 47μ axial elect. 25V |
| C4 | 10n ceramic disc |
| C5 | 220n radial elect. 25V |
| C6 | 47μ radial elect. 25V |
| C8 | 20p ceramic disc |
| C9 | 10μ radial elect. 25V |
| C10, C11, C13 | 100n ceramic disc (3 off) |

See
SHOP
TALK
page

| | |
|-----|------------------------|
| C12 | 100μ radial elect. 25V |
| C14 | 100μ axial elect. 25V |

Semiconductors

| | |
|-----|-----------------------------|
| TR1 | BC109C npn transistor |
| IC1 | LM386N audio amplifier i.c. |

Miscellaneous

| | |
|------|-----------------------------------|
| MIC1 | electret microphone insert |
| S1 | min s.p.s.t. toggle switch |
| SK1 | 3.5mm jack socket |
| B1 | 9V battery (PP3 type), with clips |

Stripboard 25 holes × 9 strips; stripboard 30 holes × 14 strips; control knob; parabolic dish (see text); metal case (110mm × 75mm × 60mm); copper tubing, standard type, approx. 15mm diameter × 100mm; mounting clip for tubing (see text); nuts and bolts as required; connecting wire; solder pins, solder, etc.

Approx. Cost
Guidance Only

£10

excl batt &
hardware

the output. There should also be a low level hum at the output, confirming that the amplifier is working. Once the amplifier has been proved, the preamplifier can be connected to it.

Key test voltages are shown in Table 2 and can be measured with a multimeter. Initially check if the microphone is picking anything up by gently tapping it and hearing the output. The prototype easily picked up ambient sound with VR1 set to less than a quarter of a turn.

Casing It

One problem encountered with circuits such as this is that they can easily pick up electrical interference, including odd (but strangely untraceable!) vibrations.

This was remedied by housing the circuit in a metal case, with the microphone situated in a copper tube (see later). Alternatively, plastic tubing with metal tape wrapped around it will suffice.

Before mounting the boards in the case, first drill the necessary holes in it and secure the copper tubing. As Fig.5 shows, the latter can be attached fairly robustly to the case with the help of a mounting clip as used in plumbing installations.

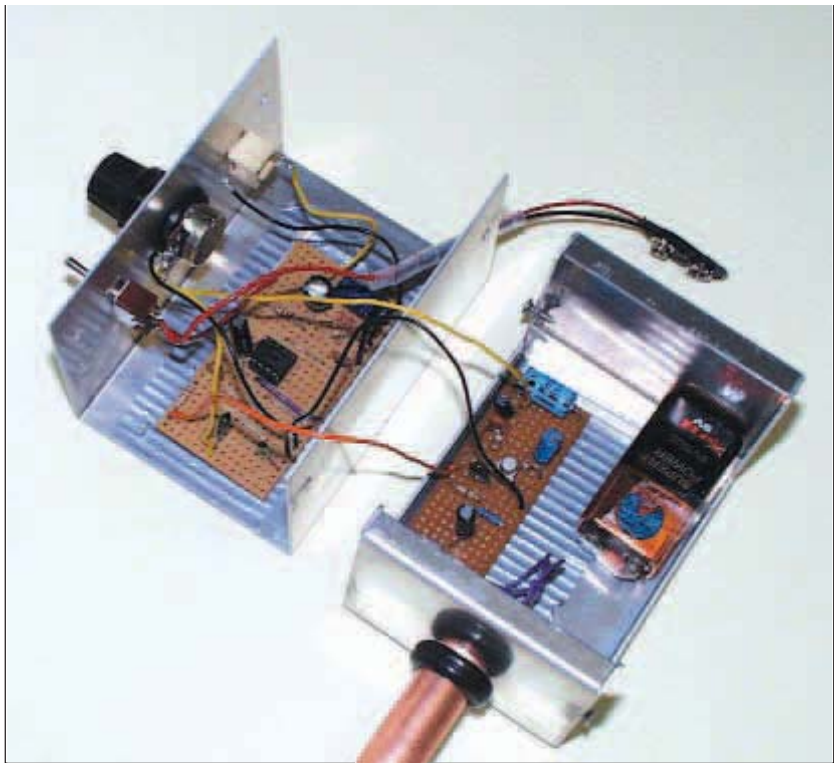


Table 2. Key Test Voltages

| | |
|---------------------------|------|
| Pre-amp supply line | 3.8V |
| Voltage across microphone | 3.1V |
| TR1 base | 0.2V |
| TR1 collector | 3.1V |
| IC1 pin 5 | 4.5V |

Assuming a 9V supply (error $\pm 0.1V$)

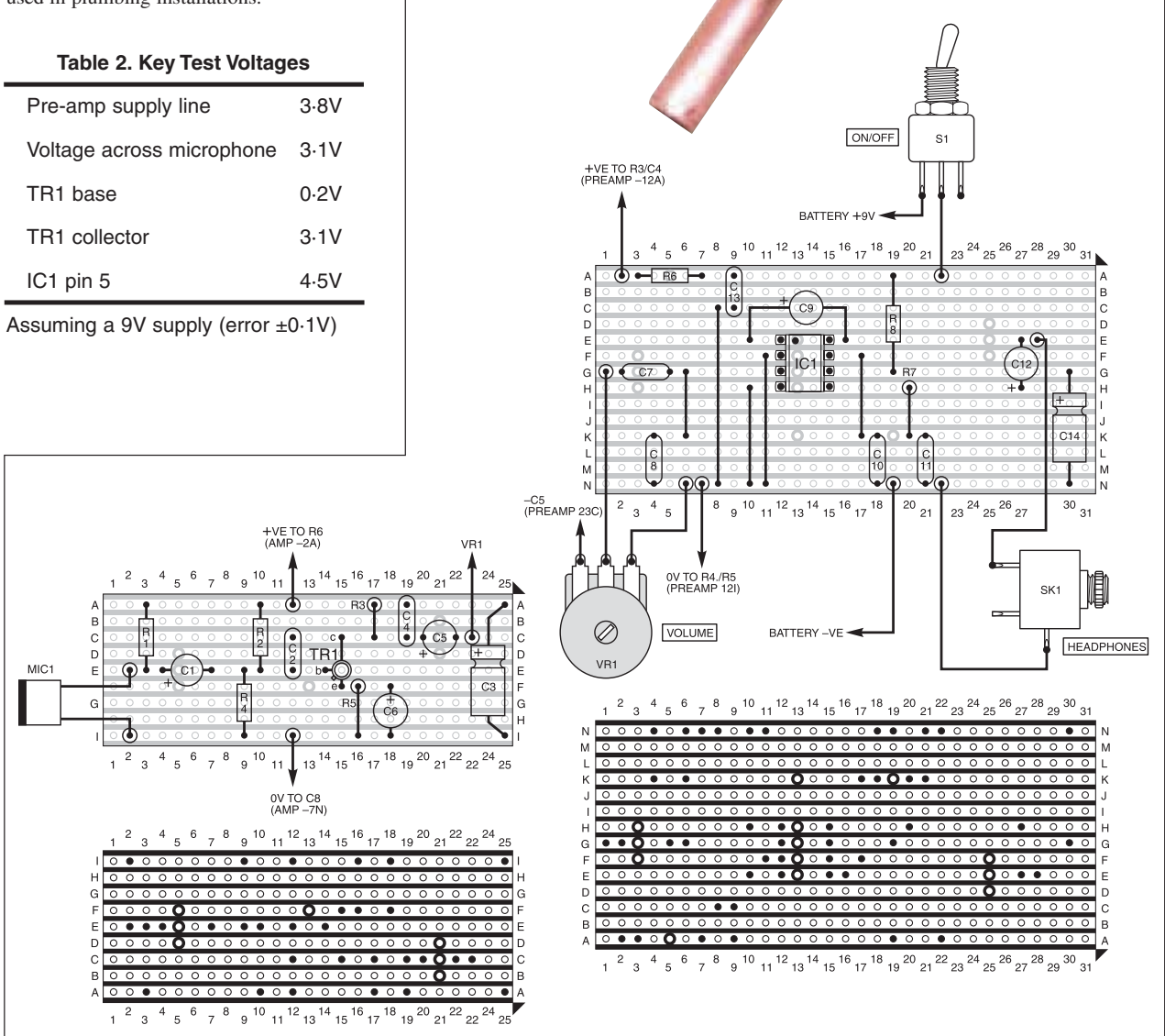


Fig.3. Super-Ear Audio Telescope stripboard component layouts, interwiring and details of breaks required in the copper tracks of the preamplifier and amplifier boards. The wiring and positioning of the two boards within the two-piece aluminium case is shown in the above photograph

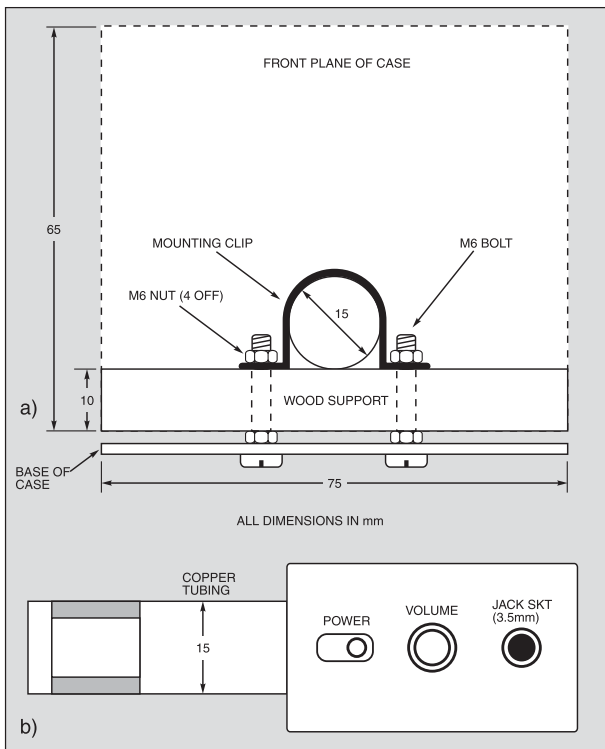


Fig.4. Securing the copper tubing, housing the mic. insert, inside the metal case (a) and (b) position of off-board components on one side panel

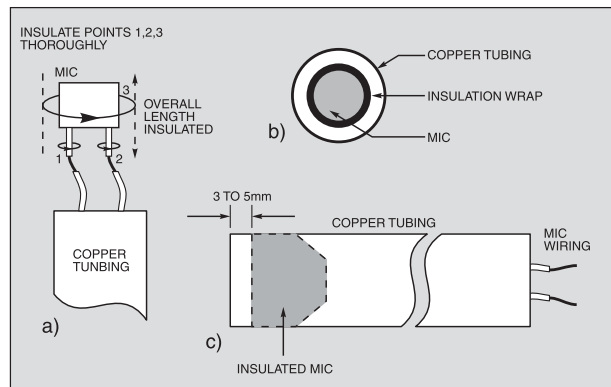


Fig.5. Insulating and wiring the microphone insert (a), end view showing insert "plugged" into the copper pipe (b) and the Mic. insert recessed in the copper tubing (c)



Electret Mounting

Because the circuit is extremely sensitive, anything picked up by the microphone can result in an ear-splitting whine dominating the output. This can be resolved by thoroughly insulating the microphone's bare metal surface using insulating tape. Handle the microphone

carefully to avoid damaging its pins. Solder the connecting cable to the pins and, as shown in Fig.5, wrap tape around each of them.

Push the cable through the copper tubing until it emerges from the other end. Now apply further rounds of tape over the microphone's case, leaving the pick-up

surface free. The microphone can then be eased into the tubing to around 3mm to 5mm short of the rim. For a snug fit and to prevent loosening, apply further rounds of tape.

Parabolic Matters

As mentioned earlier, almost anything concave and reflective to sound will boost the pick-up power of the microphone, it does not have to be a true parabola. The shape includes items such as aluminium bowls, old style car hub caps, and disused satellite dishes.

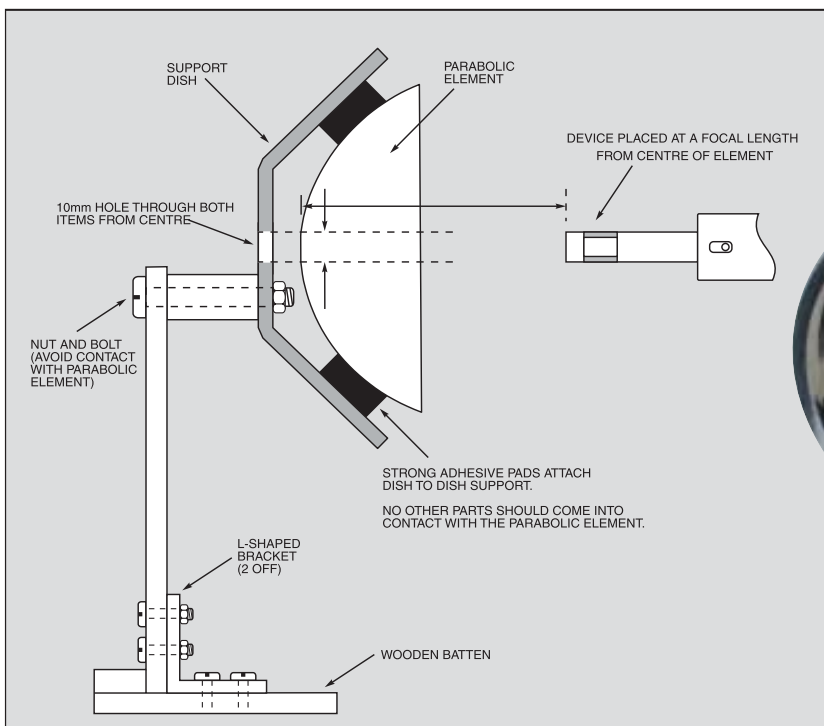


Fig.6. Suggested method for constructing a cradle/support for mounting a bigger more robust parabolic element (dish)





Ideally Super-Ear should be suspended within a framework of struts to align with the centre and focal point of the dish for optimum audio pick-up

In Use

In use, some degree of experimenting is required providing ambient noise does not block out the targeted audio.

Point the reflector dish in the general direction of interest. As shown in Fig.6, hold the Super-Ear unit *in front* of the reflector. For optimum pick-up determine the focal length for the chosen "dish", i.e. the distance at which the microphone is held from the centre of the reflector.

A trial and error method sufficed for the prototype, with interesting results. Using this method, low level sounds (only just audible but unintelligible) were amplified using

an aluminium bowl of diameter 200mm as the parabolic element, and having a focal point of 90mm.

Of course, the larger the dish diameter (typically up to 800mm) and the more parabolic the shape, the stronger the illumination. The gain of a


satellite dish antenna, for example, increases six decibels simply by doubling its size.

Because holding the parabolic element can muffle sound pick-up, it is worthwhile mounting it on a simple support via strong adhesive pads or glue such as Araldite.

Avoid using fixtures which involve drilling holes, except for the 10mm centre hole mentioned earlier. For bigger and heavier parabolic elements, the suggested method of home assembly as shown in Fig.6 can be used rather effectively.

Acknowledgements

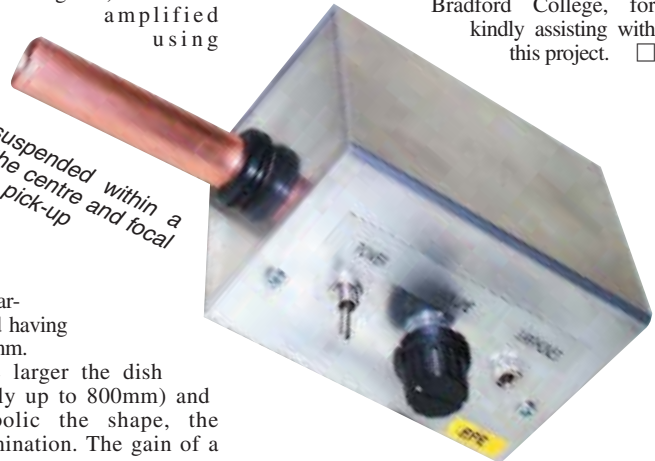The author offers many thanks to Ralph Turner and Dave Moran at Bradford College, for kindly assisting with this project. □



Drill a hole at the centre of the element equivalent to the diameter of the microphone, in this case 10mm. In terms of picking up sound this helps redirect the sound "illumination" relative to the size of microphone.

PLEASE ENSURE YOU TELEPHONE TO CHECK AVAILABILITY OF EQUIPMENT BEFORE ORDERING OR CALLING.

MISCELLANEOUS CLEARANCE STOCK

| | | |
|---|---|--|
| OSCILLOSCOPES | POWER SUPPLY Model 12030 0-20V 0-30A - On Wheels £95 | RACAL 9901 Universal Counter Timer DC-50 MHz £15 |
| TEKTRONIX 465B Dual Trace 100 MHz Delay fitted into 19in. rack frame £125 | HARMER SIMMONS 50/25/110 Input 240V 10A Output 50V 25A £100 | RACAL 9900 Universal Counter Timer 30 MHz DC-30 MHz £15 |
| HP 1740A Dual Trace 100 MHz delay (no lock) £40 | CENTRONIC M100 Repairkit Input 240V 250 VA Output 240V 1000VA £50 | WAVETEK 136 VCO/VCA Generator £20 |
| HP 1740A Dual Trace 100 MHz Analogue Storage £60 | DRANETZ 606 Line Distribution Analyser £35 | HP 435A Power Meter - No lead no head £15 |
| HP 1744A Dual Trace 100 MHz Analogue Storage £60 | WAYNE KERR B601 Radio Frequency Bridge £25 | HP 403B AC Voltmeter £15 |
| PHILIPS PM3264 4 Ch. 100 MHz £125 | FEEDBACK TF4607 Transfer Function Analyser £25 | DI-LOG PR415 Phase Rotation Indicator £10 |
| HP 1744A Dual Trace 100 MHz Analogue Storage £60 | WAVEtek 52 Data Multimeter £60 | MAYWOOD D2000 Digital Indicator £10 |
| GOLDSTAR OS9020P Dual Trace 20 MHz £50 | GOULD SG200 RF Signal Generator £20 | HP 3720A HPB Extender £10 |
| GOLDSTAR OS9020P Dual Trace 20 MHz £50 | CHATILLON Force Meter £15 | HATFIELD 2115 Attenuator 75ohm 100dB £10 |
| IWATSU SS5702 Dual Trace 20 MHz £40 | ALFRED E105 Variable Attenuator 4-80Hz £20 | HATFIELD 2115R Attenuator 75ohm 100dB £10 |
| KIKUSUI COS9020 Dual Trace 20 MHz £40 | CAMMETRIC 6 Decade Resistance Box £15 | HATFIELD 2118R Attenuator 750ohm 100dB £10 |
| | SULLIVAN C8710 Precision 5 Decade Capacitor Box £20 | HATFIELD 2135 Attenuator 600ohm 100dB £20 |
| | MARCONI 6033/3 Waveguide £20 | TEKTRONIX 1103 Tekprobe Power Supply £10 |
| | MARCONI 2169 Pulse Modulator £20 | SYSTRON DONNER 6243A Freq Counter 20Hz-1250 MHz £35 |
| | MARCONI 2430A Frequency Meter 80MHz £30 | LEVELL TG301 Function Generator 1 MHz Sine/Sq/Tri £30 |
| | MARCONI 6950 RF Power Meter - No head £35 | SOLARRON 7045 Digital Multimeter £30 |
| | MARCONI 6960 RF Power Meter - No head - Digital £50 | HP 8404A Levelling Amplifier £15 |
| | HP X382A Variable Attenuator Waveguide £20 | HP 8455A Digital Voltmeter £50 |
| | HP S316A Counter £50 | FEEDBACK FM610 Digital Frequency Meter £25 |
| | HP 8750A Storage Normalizer £20 | FARNELL TM8 True RMS RF Millivoltmeter £40 |
| | HP 907A Co-axial Sliding Load £20 | THURLBY 1503 Digital Multimeter £15 |
| | PROGRAMMA TM2 Timer £20 | SULLIVAN 6666 Milliohmeter £15 |
| | RACAL 9008 Modulation Meter £40 | K&L Tunable Bank Reject Filter £15 |
| | RACAL 9009A Modulation Meter £50 | BARR & STROUD EF-4-01 Bank Pass Filter 1Hz-100KHz £15 |
| | TEXCAN SASO 102dB in 1dB steps £15 | BARR & STROUD EF-4-02 LPHF Filter 1Hz-100KHz £15 |
| | RIRD 8341-200 Coaxial Attenuator 20dB 40W 50ohm £25 | FLUKE 8810A Digital Multimeter £25 |
| | BIRD 61 Wattmeter 6 & 30W 50ohm 30-50MHz £40 | ELUKE 8802A Digital Multimeter £25 |
| | TELEONIC TT190-5-SEE Tunable Band Pass Filter £20 | FLUKE VISUAL VU14 Waveform Monitor £20 |
| | TELEONIC 190-3EE Tunable Bank Reject Filter 125-250 £15 | TRACER NORTHERN TM1750 £30 |
| | TELEONIC 95-3EE Tunable Band Reject Filter 60-126 £15 | RS 555-279 UV Exposure Unit £10 |
| | HELPER INST CML1 Sine/DC £30 | MICRODYNE CORP. Receiver £60 |
| | HELPER INST S103 Sine/DC 3 £30 | VARIAN V2L-6941F1 Travelling Wave Tube Amplifier £50 |
| | SXP100 Parallel to Serial Converter £10 | MOORE READ SFC5001 AUXR Static Frequency Converter 120 Volts 400 Hz £50 |
| | MICROMASTER LV £40 | DRAGER 2101 Multi Gas Detector £10 |
| | DATAMAN S3 Programmer £50 | PHILIPS PM827B Multipoint Data Recorder £20 |
| | SOUTHERN CALIFORNIA BTXRM-S10 2000.0 MHz £50 | ENDECO 4417 Signal Conditioner X 2 £10 |
| | MOTOROLA R2001D Communication System Analyser £250 | PULSETEK 132 DC Current Calibrator £30 |
| | WESTON 1149 Standard Cell 1.01859 ABS Volts at 20C. £10 | PH109B-D14 Display with 1038-N10 Network Analyser. No Head £10 |
| | MUIRHEAD A-6-B Resistance Box £50 | MEGGER M4M4M2 Wind Up 1000V Mohm £50 |
| | RACAL 9917A UHF Frequency Meter 10Hz-560 MHz £45 | METROHM 250V Pat Tester £15 |
| | RACAL 9917B UHF Frequency Meter 10Hz-560 MHz £40 | SULLIVAN AC1012 4 Decade Resistance Box 0.005% £10 |
| | RACAL 9915M UHF Frequency Meter 10Hz-520 MHz £50 | BRANDENBURGH Q20 Static Freq Converter 110/240V input 50/60Hz Output 115V 400Hz 20VA £40 |
| | | NARDA 706 Attenuator £10 |
| | | ANALOGUE ASSOCIATES X800 Audio Amplifier 800watt 400p sec Channel no DC Protection £30 |
| | | W&G PC62 POM Channel Generator £30 |
| | | SIVERS LAB 12400 - 18000 MHz £10 |
| | | SIVERS LAB 5212 2500 - 4000 MHz+C264 £10 |
| | | CROPICO VS10 DC Standard 10V £30 |

EXTRA SPECIAL OFFERS

| | |
|---|--------|
| H.P. 8560A Spectrum Analyser, 50Hz-2.9GHz | £3,250 |
| H.P. 8569B Spectrum Analyser, 10MHz-200MHz | £1,500 |
| MARCONI 2382 Spectrum Analyser, 20Hz-400MHz | £1,250 |
| TEKTRONIX 2465A Oscilloscope, 4-ch, 350MHz | £750 |
| TEKTRONIX 2248 Oscilloscope, 4-ch, 100MHz | £375 |
| H.P. 8640A AM/FM Signal Gen, 500kHz-512MHz | £175 |

SPECIAL OFFERS

| | | |
|---|---------------------------------------|------|
| OSCILLOSCOPES | LECRYO 9400A dual trace, 170MHz, 5G/S | £500 |
| LECRYO 9400 dual trace, 125MHz | £400 | |
| TEKTRONIX 468 dual trace, 100MHz, digital storage | £300 | |
| TEKTRONIX 475 dual trace, 200MHz, delay sweep | £250 | |
| TEKTRONIX 465B dual trace, 100MHz, delay sweep | £250 | |
| TEKTRONIX 465 dual trace, 100MHz, delay sweep | £175 | |
| PHILIPS PM3217 dual trace, 50MHz, delay sweep | £150 | |
| THURLBY PL3200MD 0-30V 0-2A twice digital PSU | £160 | |
| H.P. 86312A 0-20V 0-2A Communications PSU | £200 | |
| H.P. 8626A Precision High Resolution PSU, 4 outputs, 0-7V 0-15A or 0-50V 0-0.5A twice, 0-16V 0-0.2A or 0-30V 0-2A twice | £500 | |
| ORRUS CR1254 Sound Level Meter with calibrator 80-120db LED | £95 | |
| WAYNE KERR B424 Component Bridge | £50 | |
| RACAL 9300B True RMS Voltmeter, 5Hz-20MHz usable to 60MHz, 10V-316V | £50 | |
| RACAL 9300B True RMS Voltmeter, 5Hz-20MHz usable to 60MHz, 10V-316V | £50 | |
| AVO DA116 Digital Avometer with battery and leads | £20 | |
| FARNELL LFMA Sine/Sq Oscillator, 10Hz-1MHz, low distortion TTL output amplitude meter | £75 | |
| FARNELL J3B Sine/Sq Oscillator, 10Hz-100kHz, low dist. | £50 | |
| HEME 1000 LCO Clamp Meter, 0-1000A, in carrying case | £35 | |
| FLUKE 77 Multimeter 3 1/2 digit handheld with battery & leads | £45 | |
| KENWOOD FT176 2-Channel Multivoltmeter | £50 | |
| KENWOOD FL140 Wow and Flutter Meter | £50 | |
| KENWOOD FL180A Wow and Flutter Meter | £75 | |
| METROHM M4M4M2 Wind Up 1000V Mohm | £25 | |
| MARCONI 6960B Power Meter with 6920 head, 10MHz-20GHz+2450 | £250 | |
| SOLARTRON 7150 DMM 2 1/2-digit True RMS IEEE | £75 | |
| SOLARTRON 7150 Plus AS 7150 - temp. measurement | £100 | |
| IEEE Cables | £5 | |
| N.P. 3312A Function Gen, 0-1Hz-13MHz, AM/FM Sweep/Sq/Tri/Burst etc. | £200 | |
| H.P. 3310A Function Gen, 0-0.00Hz-6MHz, Sine/Sq/Tri Ramp/Pulse | £80 | |
| RACAL 9008 Automatic Modulation Meter, 1-5MHz-2GHz | £60 | |
| ISOLATING Transformer, input 250V, output 500VA, unswitched | £30 | |
| RACAL 1792 Receiver | £25 | |

STEWART of READING

17A King Street, Mortimer, Near Reading RG7 3RS
Telephone: (0118) 933 1111. Fax: (0118) 933 2375
www.stewart-of-reading.co.uk

Open 9am-5.00pm Monday to Friday (other times by arrangement)



Used Equipment - GUARANTEED. Manuals supplied

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists.

Please check availability before ordering.

CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage