

Digital Generation of LFO's for Modulating Effects

Copyright 2000 R.G. Keen. All rights reserved. No permission for local copies or serving from web sites other than <http://www.geofex.com>.

[\[PseudoRandom LFO\]](#) [\[Star Stepped LFO\]](#) [\[Other Digital LFO Waveforms\]](#) [\[An Analog Sequenced LFO\]](#)
[\[Connecting the LFO's up to Effects\]](#)

Modulated effects are pretty neat, but after you've been around a phaser or flanger swooshing repeatedly back and forth for a long time, you get fairly bored with the predictability of the effect. To liven things up a bit, add a little unpredictability to modulated effects with a pseudorandom modulation.


Paraphrasing Dr. Hook and the Medicine Show "pseudorandom? Oh, wow, man... what's that??". "Pseudo" means something like "looks like but isn't the real thing". So a pseudorandom signal looks like - but isn't exactly - a random signal. It turns out that real random signals are very, very hard to produce reliably. Fortunately, you don't have to make things perfectly random to be pleasing to people; in fact, some regularity is quite pleasing, as long as there is some variability in it.

There are some logical counter techniques that can product very convincing simulations of real random signals. The so-called "maximum length sequence" counters do a pretty good job of this. However, they're a bit too complicated and even too random for most musical uses. A simpler, and perhaps more pleasing pseudorandom generator can be made simply from several square wave oscillators.

One square wave oscillator isn't random at all - it just bangs back and forth regularly. If we take a second oscillator running at a very slightly different frequency, we get the classical "beating" between the two. This is familiar to every guitarist who hears beats between notes as he tunes up his axe. Still very predictable, though. Adding a third oscillator starts to mix things up, though. Now there are two beats wandering around as well as the original oscillator frequencies. This has an amount of randomness about like ocean waves, and a three-oscillator LFO was actually used for a surf-sound synthesizer by PAIA in one of their kits. A fourth oscillator takes you over the cliff to pretty darn unpredictable in the short run, but with some recognizable similarities over long times.

Pseudorandom LFO

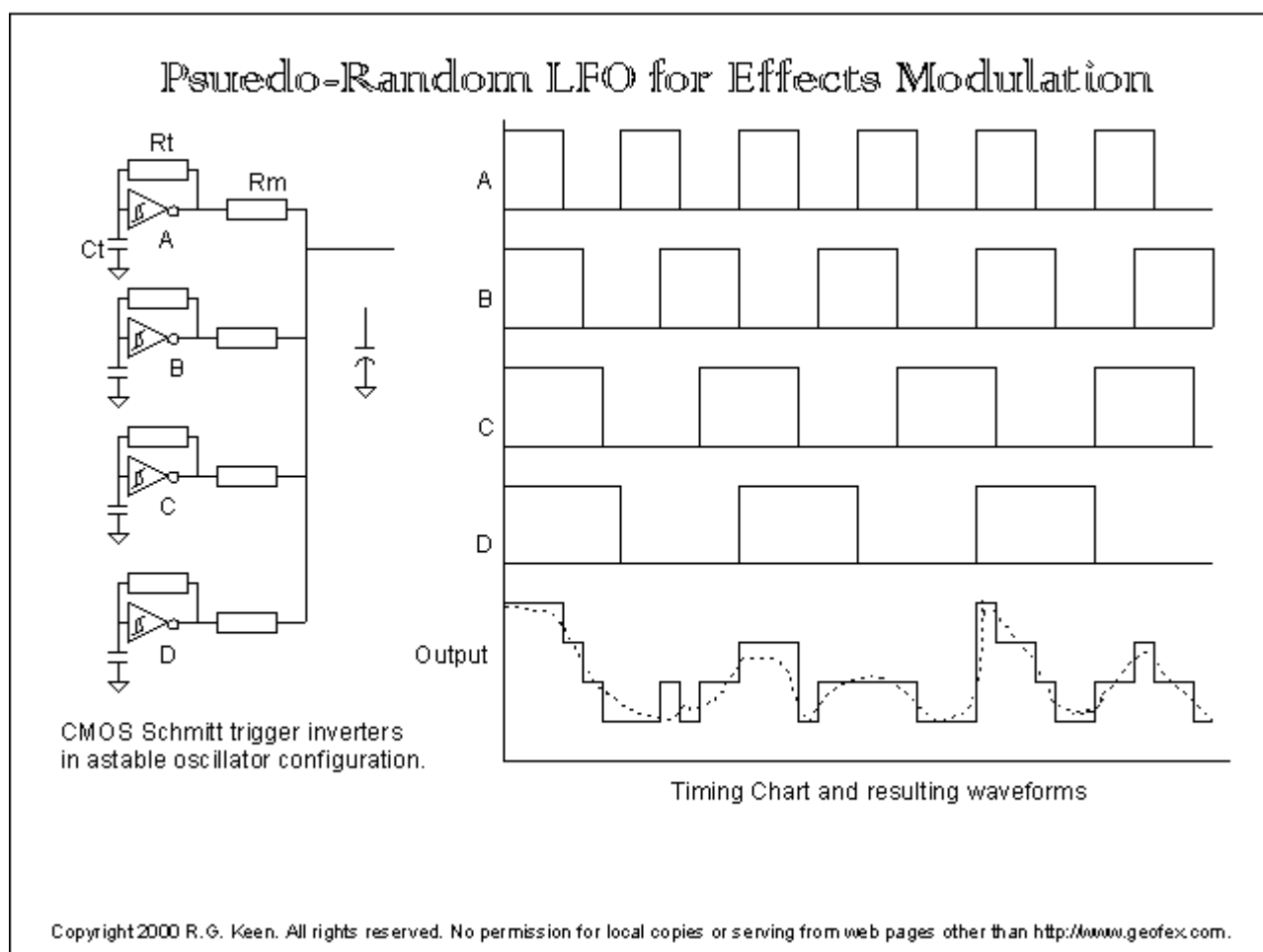A very quick
and easy way to
make a multiple
oscillator
pseudorandom
LFO is shown
in the
illustration.
Schmitt trigger
CMOS inverters
like the
CD40106, CD
4584, and
others make
easy oscillators.
They have
hysteresis, so if
you feed a
capacitor from
their output
through a
resistor and
connect their



input to the

capacitor/resistor junction, the gate alternately charges and discharges the capacitor, providing a square wave on the inverter's output.

The timing chart shows how the randomness works. I've shown four oscillators, mixed with four resistors.

When the power is turned on to the chip, all the capacitor are at 0V, so the outputs are all high. The capacitor voltage ramps up through the feedback resistor, R_t . Since all the oscillator outputs are high, the output is as high as it can go (usually the power supply voltage). When the fastest oscillator, A in this case, flips to its most negative state, it pulls the output down a bit, but the other three hold it up to about 3/4 of the max value. When the second oscillator changes state, the output drops another step.

What's most interesting is that as the oscillators run, they go through all possible reinforcing and interfering states. I've plotted out some possible results in the illustration. The output comes out as a kind of drunken, staggering stairstep waveform. If you connect a smoothing capacitor to the output, it smooths the rough edges off the stairsteps, and the output becomes a smooth, but still staggering wave like the dotted line.

Both the stairstep and smoothed version are useful. A filter like a wah modified to be controlled by an external signal (See "The Technology of Wah Pedals") would leap from one resonance point to the next in a not-very predictable way if controlled by the drunken stairstep. It would swoop around unpredictably if fed by the smoothed version.

Notice that while the output waveform does occasionally get as large as the full supply voltage and as small as 0V, that it spends most of its time near the middle of the power supply. In applying this LFO, you may need to adjust the DC level up or down to suit the element of the circuit that you are controlling. A resistor to ground will lower the peak voltage from V_{supply} down to $V_{supply} * (R_{||} / R_{pull-down})$ where $R_{||}$ is the parallel combination of all the mixing resistors R_m , and $R_{pull-down}$ is the added resistor. A resistor to a decoupled V_{bias} in the middle of the power supply will simply reduce the peak to peak size of the LFO waveform, but leave its average level the same. A resistor to the positive supply will make the LFO output a maximum of the supply voltage, but will reduce the peak to peak size in the same way the pull down resistor did, so the variation will all be smaller and near the power supply voltage.

Regular Stair Step LFO

For non-random LFO waveforms, we need a non-random way to generate them. A really handy way to do this is with a walking ring counter. Figure 1 at the right shows one way to do this.

The counter is a series of D-type flipflops all clocked by a common clock. A "D" flipflop accepts whatever logic level is present at its D (for "data") input when the clock ticks and latches that into its "Q" output. With a string of these things, the logic level that appears at the D input of the first flipflop will be passed down the line, one flipflop per clock tick.

What makes it a "walking ring" is that the output of flipflop E is inverted and fed back to the D input of flipflop A..


When the power is first turned on, before the first clock tick, we'll assume that the flops are all sitting at "0". That means that the inverter has a 0 on its input from the output of E, and is presenting a 1 to the D input of flipflop A..

On the first clock tick, the 1 on the first D input is transferred to the Q of the first stage. All of the other flipflops saw a 0 on their D inputs, so they clocked in a 0 - effectively no change. The inverter still sees a 0, so it still puts a 1 on the first D input. On the second clock tick, The first stage clocks in another 1, but the second stage now clocks in the 1 from the first flipflop's Q output. The remaining three flipflops still clock in a 0.

On each clock tick, a 1 is clocked into the first flipflop, and the chain of flipflops fills up with 1 logic levels from the left. This keeps happening until the last flipflop gets a 1 clocked into its output. At that point the inverter puts a 0 on the D input of the first flipflop.

A string of five ones has been clocked into the counter. When the counter fills with ones, it then fills with 0s. This series of counting will continue forever, with the counter filling alternately with 1's and then 0's.

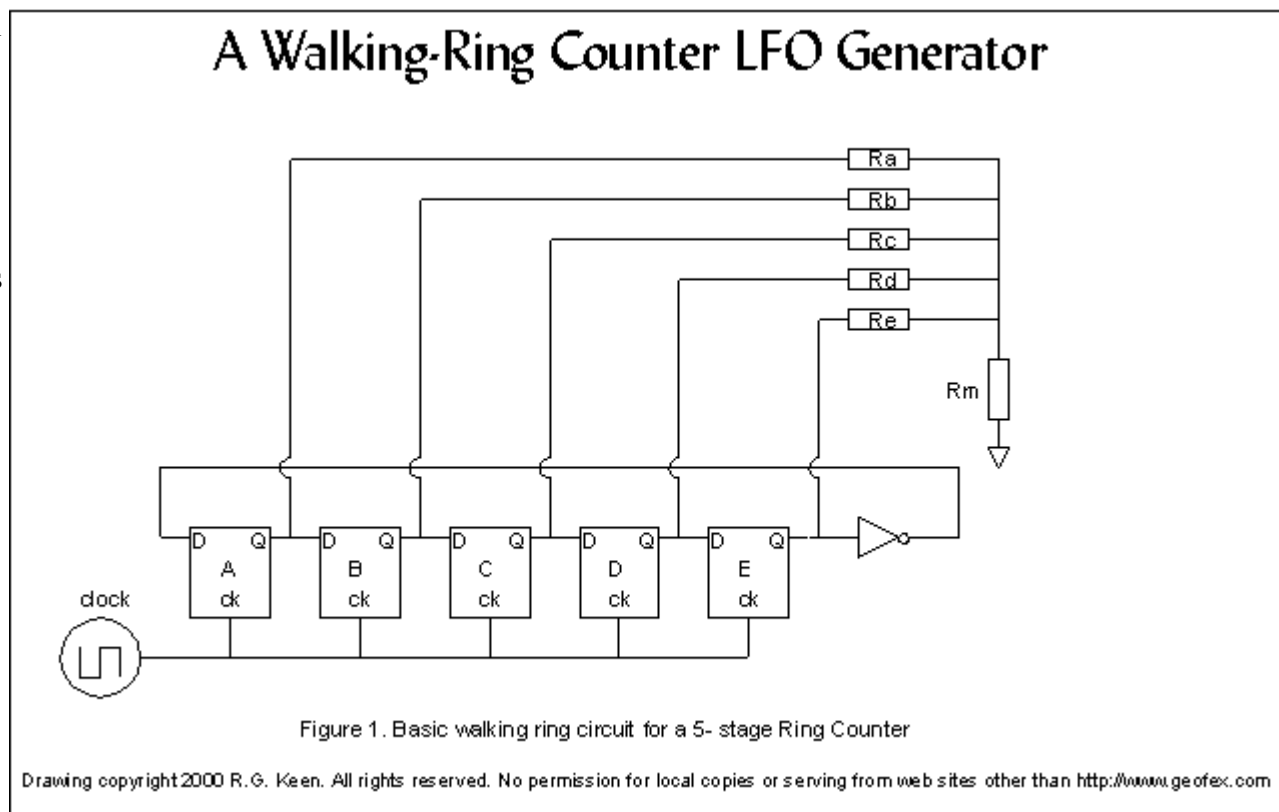What makes this useful is that we can use the overlapping nature of the outputs to generate waveforms. Figure 2 shows how this works. With each clock tick, the



A Walking-Ring Counter LFO Generator

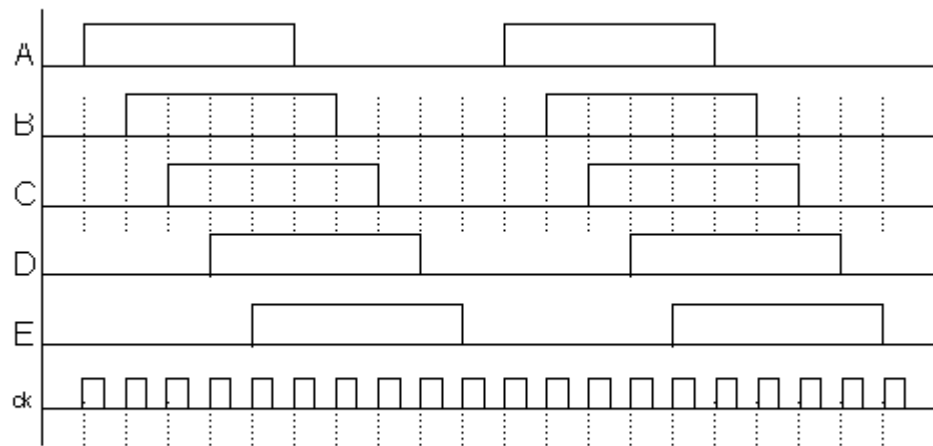


Figure 2. Outputs of the flipflops in the walking ring counter.

Drawing copyright 2000 R.G. Keen. All rights reserved. No permission for local copies or serving from web sites other than <http://www.geofex.com>


"bundle" of ones and 0's rotates through the set of flipflops. If we look at all the outputs simultaneously,

the set of 0's and ones at each successive clock tick looks like:

```
ABCDE
00000
10000
11000
11100
11110
11111
01111
00111
00011
00001
00000
```

If we then consider these "1's" and "0's" as analog voltages, we can use resistors to add them up and make different waveforms from them.

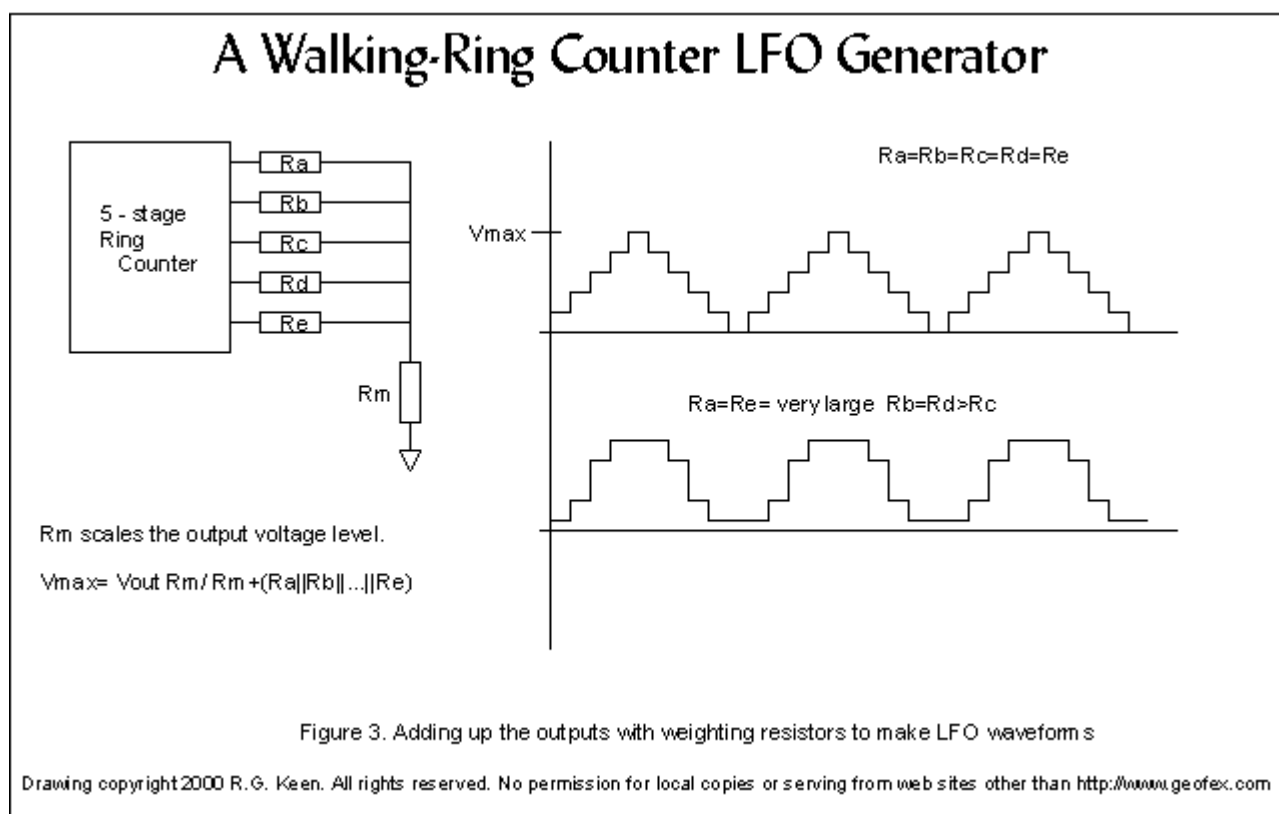The simplest thing to do is a stairstep. As we see in figure 3, we can put an equal resistor in series with each one, and tie all of those to a "mixing resistor" R_m . With all of the outputs at 0, the voltage across R_m is also 0. With one of the outputs at 1, the voltage across R_m is just



determined by the resistive voltage divider formed; one

resistor is effectively connected to the supply voltage (with CMOS logic, anyway) and the second resistor is R_m in parallel with all the other output resistors, as they're all held at 0 as well. Two outputs high gives a next step up, and so on until all the outputs are high, giving the maximum output for the waveform. For the five stage ring counter we've been using for an example, you get the neatly stepped waveform shown at the top.

Other Digitally Generated LFO's

But the resistors don't all have to be equal, do they? In fact, you can make a pretty good sine wave by making the "middle" resistor smaller than the others, and having the values of the resistors calculated to make the closest approximation of a sine wave at the time the clock ticks. The second waveform shows how this can be done. The non-uniform steps make an ugly approximation to a sine wave. If you are careful about selecting the resistor values and filter the output with even a simple capacitor, the approximations start to look VERY much like a sine wave. With a large number of stages in the walking ring counter, you can approximate a sine wave to any degree you'd like.

More on digital sine waves in a later update!

Implementing the CMOS Walking Ring Counter

"But..." I can hear you asking, "isn't all that digital stuff complicated to do and hard to put into effects?"

Maybe. Maybe not. The trick here is that a whole digital walking ring LFO circuit can be done with only two CMOS chips of the US\$0.30 variety.

Figure 4 shows one way. With the CD4015 dual four-bit shift register and one hex inverter chip, you get a walking ring counter of lengths one to

A Walking-Ring Counter LFO Generator

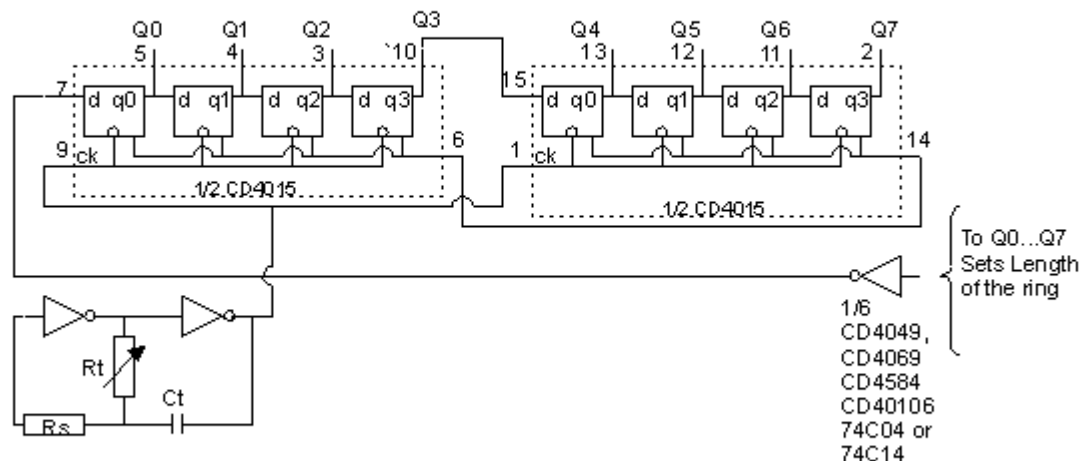


Figure 4. CMOS Ring Counters - Two CMOS chips give length one to length eight

Drawing copyright 2000 R.G. Keen. All rights reserved. No permission for local copies or serving from web sites other than <http://www.geofex.com>

eight. The length of the walking ring is really determined by where you take the feedback from. If you string the two

halves of the CD4015 together for a length-eight shift register, you only need to connect an inverter input to one of the outputs and feed the inverter to the D input on the first shift register. If you tie it to Q3, then Q0...Q3 form a length-four chain. If you tie it to Q6, you get a length-seven chain.

The necessary inverter to make the ring count and the variable speed clock to make the whole mess run only take 1/2 of a hex inverter.

This being digital, you know very exactly what will happen and when. You can play tricks with the ring counter to do other things as well:

If you tie the "reset" inputs to Q7, the ring will walk a one up through Q6 (seven steps, that is, since Q0 is the first one) and the instant that Q7 gets clocked to a 1, it resets the chip to all 0's. This happens so fast that you can't see it on a normal oscilloscope. If you connect up equally weighted mixing resistors, it looks like a staircase up for seven steps, then a sudden fall back to 0. It's a stepped sawtooth wave, in other words. You may like the steps in things like a stepped LFO, or you could smooth it out to a psuedo-linear sawtooth.

Why bother with all this? Can't I just do a LFO with opamps?


Sure you can. However, you rapidly run into some limitations. Opamp waveform generators that operate over wide ranges of frequency and hold tight control of DC levels and symmetry are tricky to do. They don't offer the option of the stairstepped waveforms at all - only the smoothly varying ones. A pulse oscillator like that needed for the clock of these things can have a much wider frequency range and still run the counters just fine, as well as operating at higher frequencies, so large timing caps are not needed. Not only that, but we'll get into some things that are difficult if not impossible to do with a reasonable amount of opamps. Here's one that you can't do with opamps, at least not very easily.

An Analog Sequenced LFO

The picture at the right offers an eight stage stepped LFO that can be any voltage at any given time. Let's look at how this works.

The CD4060 is

An Eight Stage Analog Sequencer

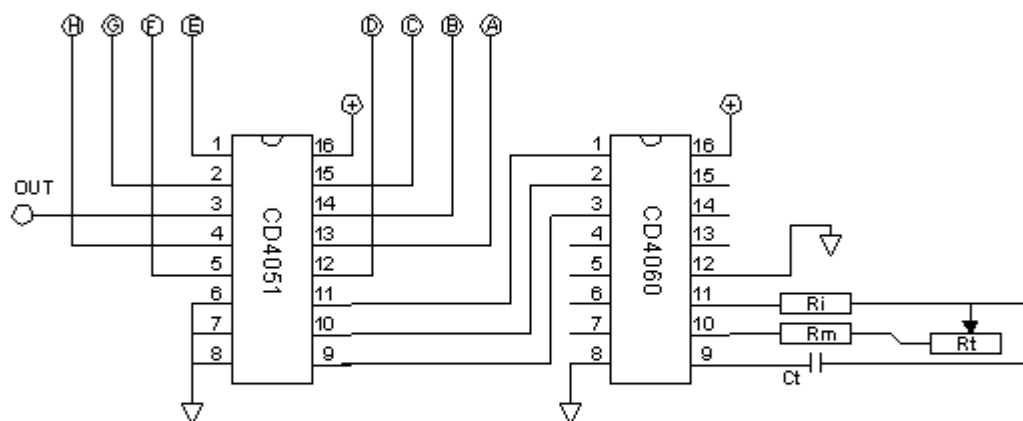

Sequencer "samples" A, B, C, ... H, A, B, C... in order forever. Sample speed is controlled by the timing components R_t , C_t , and to a lesser extent R_i , R_m . $R_m + R_t$ is the effective timing resistance, and R_m sets a maximum speed. Time between sequence steps is $16384 * 2.2 * C_t * (R_m + R_t)$. For $R_t = 50K$, $R_m = 4.7K$, and $C_t = 470pf$, step time varies between about 1 second and 1/10 second. the on-chip oscillator of the CD4060 runs between 16kHz and 160kHz, so audio interference is unlikely.

Copyright 2000 R.G. Keen. All rights reserved. No permission for local copies or serving from sites other than <http://www.geofex.com>.

a CMOS 14-stage binary counter with an internal oscillator on chip. The oscillator is controlled by the resistors and capacitor tied to the timing pins, 9-11. This oscillator runs the binary counter, and the various outputs count at the oscillator speed. In particular, pins 1, 2, and 3 count at 1/16384 th of the oscillator frequency.

If we set the main oscillator to run from 16384 Hz to 163840Hz, then outputs 1,2 and 3 count at from 1 Hz to 10 Hz.

The outputs at pins 1-3 are supplied to the selector inputs of the CD4051. The 4051 is a one-of-eight analog selector switch. This is like a single pole, eight throw switch that connects one of eight positions to a single output pin. As the counting inputs change, input A, B, C, ... H are selected in turn and connected to the output on pin 3. Once H is reached, the cycle starts over at A.


The inputs to the selector chip can be any voltage within the range of the chip's positive supply pin (shown as a plus sign with a circle around it) to its most negative supply pin, shown as ground. We could connect eight potentiometers to those inputs, with the potentiometers strung between the + supply and ground. If we did that, we could adjust the voltage for each step independently, and the sequencer would select each of those in turn. The LFO output could be any of eight different values, depending only on the settings of the eight pots. There is a commercial device that does a similar operation, although I have no idea if it's implemented in the same way.

This task would be almost impossible to do with any reasonable number of opamps.

Driving Effects Circuits with the LFO Waveforms

OK, looks good, we can get some fancy modulating waveforms. How do we hook them up to effects?

The simplest

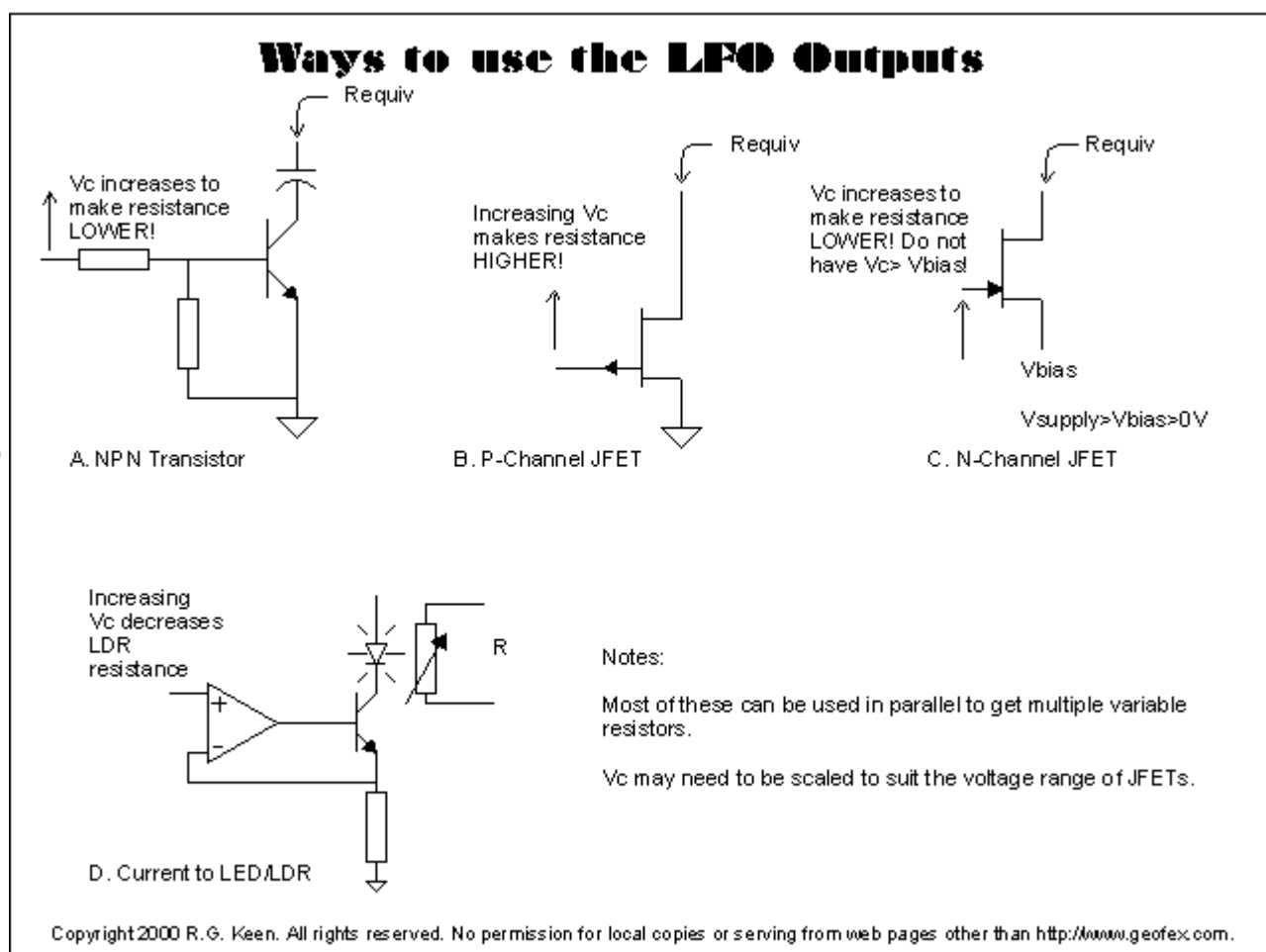

thing to do is to use either a bipolar (normal) transistor or a JFET as a variable resistor that does the actual effect modulating. This is illustrated at right.

In A. an increasing control voltage (V_c) makes the

NPN transistor turn on more. For small voltages at its collector and small base currents, this acts like a variable resistor. This is the variable resistor technique actually used in effects like the Seamount Funk Machine, EH Dr. Q, and the EH Pulsar tremolo. The trick here is to make the base current very low by making the resistance in series with the base very large. For our digitally generated LFO waveforms, the output voltage may be as low as 0V and as high as the full power supply voltage.

To control the NPN transistor, all we need to do is to note that the transistor really doesn't care what voltage is there, it only cares about the current into its base. We can simply make the R_m mixing resistors be large, maybe 100K and up, and the resistors themselves make an effective "current source" into the NPN transistor's base. If the transistor's collector resistance is connected directly to the signal lines, we need to do some housekeeping to keep things nice. A big electrolytic capacitor as shown will keep the inherent offset voltage of the bipolar transistor from being transmitted into the circuit; likewise, we probably want a capacitor of some kind from the base to emitter to slow down the very fast jumps of voltage that digital LFO's feed to the transistor base. The transistor is, after all, still an amplifier, and it will amplify those steps as well! Slow it down a bit.

With mixing resistors in the 100K and up class and a 2N5088, circuit A can be used to operate the Seamount and Dr. Q. wah filters, and the single-resistor-to-ground wahs as noted in The Technology of Wah Pedals here at GEO.

Another way to get a variable resistor to ground is shown in B. A P-channel JFET acts like a variable resistor when its gate is more positive than its source. We've shown the source grounded, and the V_c control voltage applied to the gate. Since V_c from our digital LFO's can go from ground to some positive voltage easily, this connection is also a natural. Most JFET do not need a range of 0V to 9V of V_{gs} to go from fully on to fully off, so in this case, we will likely need a pulldown resistor to decrease the size of the LFO output and make sure it never goes more negative than ground. A P-Channel JFET is fully on when its gate is the same voltage as its source, and has a higher and higher resistance as its gate gets more positive; this is the reverse of the NPN transistor, so a larger V_c turns a P-channel JFET more OFF (higher resistance) while a larger V_c turns an NPN transistor more ON (lower resistance).

An N-channel JFET is also a good variable resistor, and that is what is used in many effects circuits. It gets a bit trickier though, because an N-channel JFET wants its gate to go more negative than its source to make it higher resistance. So we have to pin its source to some intermediate DC voltage like a V_{bias} source, and then vary the

gate voltage lower than that. Again, we probably want a pull-down resistor, but we need to diddle the value to get the peaks of the LFO waveform to hit $V_{gs}=0$ (fully on) and to go negative enough to make the JFET a high enough resistance.